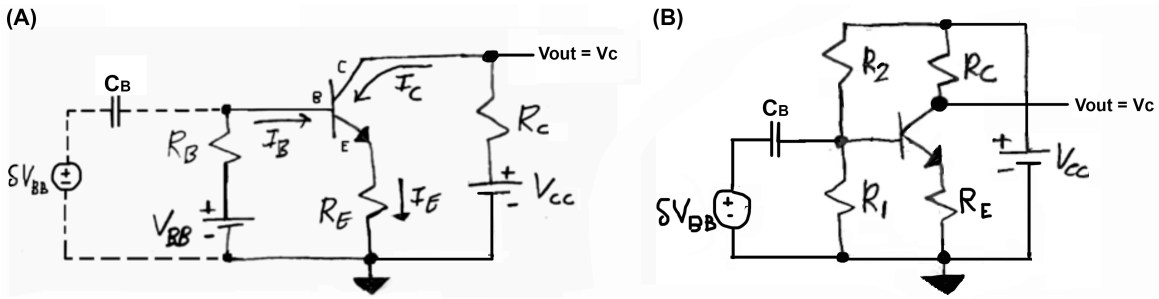


Your name:

Your student number:

Physics 120 - Final exam - 14 June 2018

Complete the design of the common emitter transistor amplifier using a 2N3904 NPN BJT, demonstrate that it operates as planned in terms of gain, dynamic range, and bandwidth.



The left hand loop (**Fig. A**)

$$-V_{BB} + I_B R_B + V_{BE} + I_E R_E = 0$$

but $I_B = \frac{1}{\beta} I_C$ and $I_E = \frac{1+\beta}{\beta} I_C$

so $I_C = \frac{\beta}{1+\beta} \frac{V_{BB} - V_{BE}}{R_E + R_B/(1+\beta)}$

Recall that $\beta \gg 1$ ($\beta \sim 100$ in this case) and choose $R_B \ll (1+\beta)R_E$. Then

$$I_C \approx \frac{V_{BB} - V_{BE}}{R_E}$$

Gain: The output voltage is given by

$$V_C = V_{CC} - I_C R_C = V_{CC} - \frac{V_{BB} - V_{BE}}{R_E} R_C = \left(V_{CC} + \frac{R_C}{R_E} V_{BE} \right) - \frac{R_C}{R_E} V_{BB}$$

The output is equal to the collector voltage, V_C , and is linear in V_{BB} . The voltage V_{BB} contains a constant as well as a signal component, δV_{BB} (**Fig. A,B**). The change δV_{BB} leads to a proportional change in the output, δV_C , *i.e.*,

$$\delta V_C \approx -\frac{R_C}{R_E} \delta V_{BB} \text{ where the ratio } "- R_C / R_E" \text{ is the voltage gain of the circuit.}$$

Load line: The set-point, denoted $I_{C,Q}$ and $V_{CE,Q}$, are the values of I_C and V_{CE} with $\delta V_{BB} = 0$. The value of V_{CE} is bounded at by $V_{CE,Sat} = 0.2 \text{ V}$ and $V_{CC} = 15 \text{ V}$.

Design constraints:

Choose $V_{CEQ} = V_{CC}/2$ to insure a (near) maximum voltage swing.

Choose $I_{CQ} = 10 \text{ mA}$, the optimum current for this BJT

Choose $|\text{Gain}| = 10$, so $R_C = 10 R_E$

Satisfy the load-line relation $I_{CQ} \approx \frac{V_{CC} - V_{CEQ}}{R_E + R_C} \approx \frac{V_{CC}}{2R_C}$, which yields $R_C \approx \frac{V_{CC}}{2I_{CQ}}$.

Satisfy the constraints $R_B \ll \beta R_E$. Since $\beta \geq 100$, select $R_B = 10 R_E$.

Calculate $V_{BB} \approx V_{BE} + I_{C,Q} R_E$.

Your name:

Your student number:

Realization (*note: confirm the value of all components prior to construction*)

(1a-c) Pick standard values of resistors:

$$R_C \approx 750 \Omega \quad R_E \approx 75 \Omega$$

$$R_B \approx 750 \Omega$$

(1d) Calculate V_{BB} :

$$V_{BB} \approx 1.2 \text{ V}$$

Convert from dual to single power supply with a voltage divider (**Fig. B**) to replace V_{BB} and R_B :

$$R_B \approx \frac{R_1 R_2}{R_1 + R_2} \quad \text{and} \quad V_{BB} \approx \frac{R_1}{R_1 + R_2} V_{CC} \quad \text{so that} \quad R_1 \approx R_B \frac{V_{CC}}{V_{CC} - V_{BB}} \quad \text{and} \quad R_2 \approx R_B \frac{V_{CC}}{V_{BB}}$$

(1e,f) Pick standard values of resistors:

$$R_1 \approx 810 \Omega \quad R_2 \approx 10 \text{ k}\Omega$$

(1g) Show that your choice satisfies $R_1 \ll R_{input}$, i.e., $R_1 \ll \beta R_E$, so that the input resistance does not contribute to the voltage divider.

$$810 \Omega \ll 100 * 75 \Omega = 7500 \Omega$$

Testing (*recall: the oscilloscope and DMM inputs are not differential*)

(2a) Measure and record the actual value of $V_{CE,Q}$ (how?):

$$V_{CE,Q} \approx \text{(Call for a TA to demonstrate your measurement)}$$

Differential voltage from collector to emitter. This could be successive measurements.

(2b) Measure and record the actual value $I_{C,Q}$ (how?):

$$I_{C,Q} \approx \text{(Call for a TA to demonstrate your measurement)}$$

Series current along collector OR along emitter leg OR via voltage drop across R_C or across R_E . Drop across R_E is a single probe measurement and simplest.

(2c) Pick a standard value of capacitor, or combined capacitors, to couple δV_{BB} through a high-pass filter with cut-on frequency of $f_{High-pass} \sim 1.0 \text{ kHz}$ (**Fig A,B**) (*recall: $f_{High-pass} = 1/(2\pi R_B C_B)$*):

$$C_B \approx 0.21 \mu\text{F} \quad \text{OR} \quad \text{two } 0.1 \mu\text{F} \text{ capacitors in parallel}$$

(2d) Show that the output δV_C spans the full range of positive and negative values of δV_{BB} for an $\sim 1 V_{peak-to-peak}$ sine input at $\sim 10 \text{ kHz}$ (*note: ensure $Z_{out} = \text{High}$ for the function generator*).

Call for a TA to observe your demonstration (show δV_{BB} and δV_C on the oscilloscope)

(2e) Measure the output δV_C as a function of frequency (*hint: use "AC" coupling on the oscilloscope for ease*). What is the actual value of the cut-on frequency, i.e., f_{3dB} for high-pass?

$$f_{High-pass} \approx$$

(2f) What is the value of the cut-off frequency, i.e., f_{3dB} for low-pass?

$$f_{Low-pass} \approx$$

(2g) What is the origin of the high-frequency filtering for $f_{Low-pass}$?

Your name:

Your student number:
