

Physics 120 Mid term "Cheat Sheet"

| Device | $V = f(I)$ | $I = f(V)$ | Z |
|--------|--|--|-----------------------|
| R | $V = IR$ | $I = V/R$ | R |
| L | $V = L \frac{dI}{dt}$ | $I = \frac{1}{L} \int_{0^+}^t dx V(x) + V_0$ | $i\omega L$ |
| C | $V = \frac{1}{C} \int_{0^+}^t dx I(x) + V_0$ | $I = C \frac{dV}{dt}$ | $\frac{1}{i\omega C}$ |

Convolution


$$V(t) = \int_{-\infty}^t dx \underbrace{\Phi(x)}_{\substack{\uparrow \\ \text{Solution to homogeneous equation}}} \underbrace{F(t-x)}_{\substack{\uparrow \\ \text{Drive term}}}$$

Fourier Transform

$$\hat{V}(\omega) = \int_{-\infty}^{+\infty} dt V(t) e^{-i\omega t}$$

$$V(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} d\omega \hat{V}(\omega) e^{+i\omega t}$$

Ideal Operational Amplifier

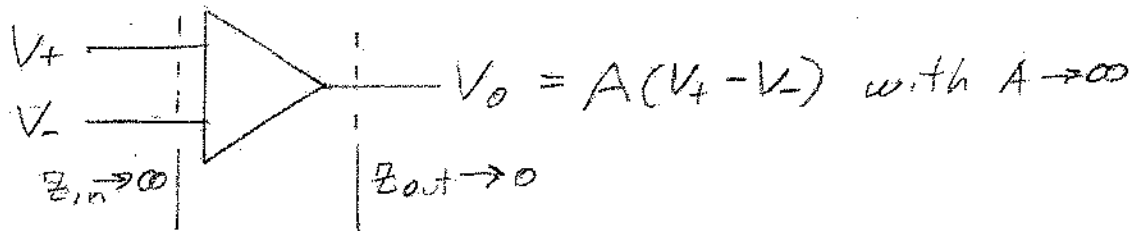

Diode

$$I_D = I_0 (e^{eV_0/k_B T} - 1) \xrightarrow{\text{Approx}} \begin{array}{c} I_D \\ | \\ 0 \text{---} 0.6V \text{---} V_0 \end{array}$$

2

Some Math Relations

Complex numbers

$$\text{Let } c \equiv a + ib$$

$$|c| = \sqrt{(a+ib)(a-ib)} = \sqrt{a^2 + b^2}$$

$$\arg\{c\} = \arctan(\text{Im}\{c\} / \text{Re}\{c\}) = \arctan\{b/a\}$$

Trigonometry

$$\sin x = x - \frac{x^3}{3!} + \dots$$

$$\cos x = 1 - \frac{x^2}{2} + \dots$$

$$\sin x = \frac{1}{2i} [e^{ix} - e^{-ix}]$$

$$\cos x = \frac{1}{2} [e^{ix} + e^{-ix}]$$

Calculus

$$\frac{d(xy)}{dt} = x \frac{dy}{dt} + y \frac{dx}{dt}$$


$$\int \frac{dx}{x} = \log x + \text{constant}$$

When $f(x) \rightarrow 0$ and $g(x) \rightarrow 0$ as $x \rightarrow 0$, then

$$\lim_{x \rightarrow 0} [f(x)/g(x)] = \lim_{x \rightarrow 0} \left[\frac{df(x)}{dx} / \frac{dg(x)}{dx} \right]$$

$$f(x-x_0) \equiv \frac{1}{2\pi} \int_{-p}^p dy e^{-j(x-x_0)y}$$


Systems

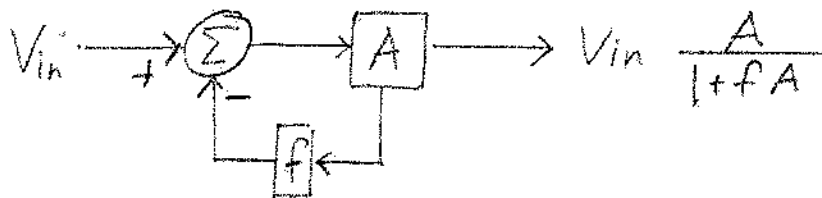

3

Physics 120 Midterm Exam (4 Problems)

①

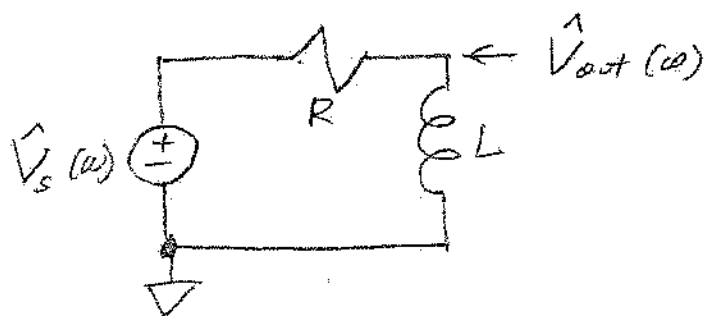


A: Write an expression for $\hat{V}_{out}(\omega)$ in terms of $\hat{V}_s(\omega)$, R , and L .

B: Sketch a Bode plot, with labeled slopes and "break" frequencies (or frequency), i.e.,

B1: $\log |\hat{V}_{out}(\omega)/\hat{V}_s(\omega)|$ vs. $\log \omega$

B2: $\arg\{\hat{V}_{out}(\omega)/\hat{V}_s(\omega)\}$ vs. $\log \omega$

②

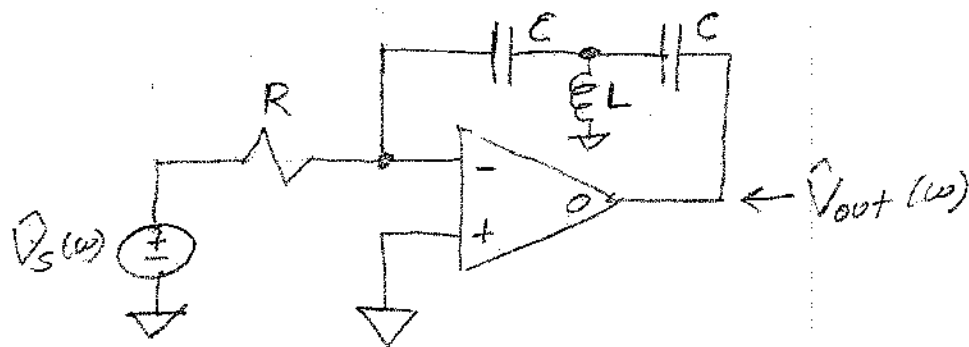

A: Write an expression for $\hat{V}_{out}(\omega)$ in terms of $\hat{V}_s(\omega)$, R , L , and C . Assume an ideal op-amp.


B: Sketch a Bode plot, as in problem 1

C: Is there a frequency for which $\hat{V}_{out}(\omega) = 0$? If so, what is that frequency in terms of R , L , and/or C ?

4

3


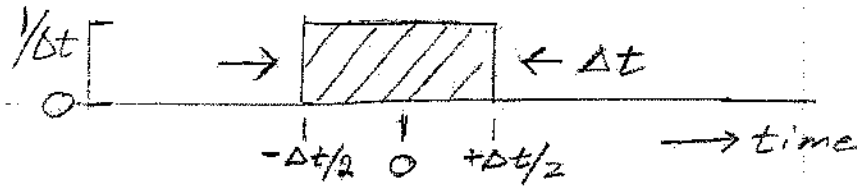
A: What is the Fourier transform, $\hat{V}(\omega)$, of a pulse of width Δt and height $1/\Delta t$?



$$V(t) = \begin{cases} 0 & \text{if } t < -\Delta t/2 \\ 1/\Delta t & \text{if } -\Delta t/2 < t < \Delta t/2 \\ 0 & \text{if } t > \Delta t/2 \end{cases}$$

B: What is the form of the Fourier transform in the limit $\Delta t \rightarrow 0$?

4

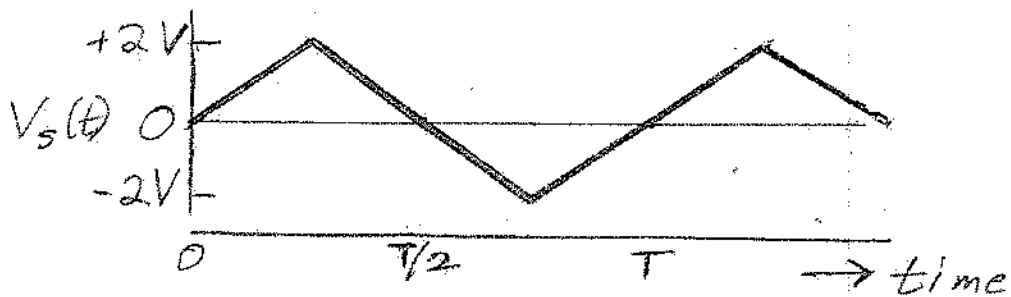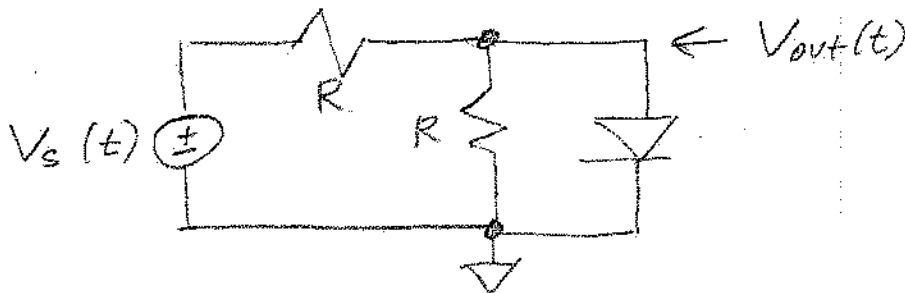

A: Plot the form of $V_{out}(t)$. Assume the diode is an ideal diode in series with a 0.6 V source. Label your axes and label all voltage levels clearly.