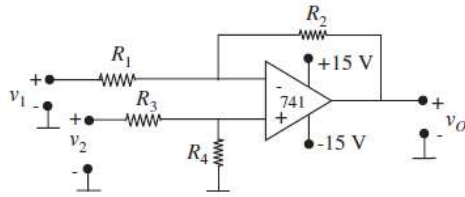


Homework 4

Thursday, April 27, 2017 1:25 PM

Ex 15.4)



a. $V_+ = \frac{R_4}{R_3 + R_4} V_2$ voltage divider

$$\frac{V_1 - V_-}{R_1} + \frac{V_0 - V_-}{R_2} = 0$$

$V_0 = V_- - \frac{R_2}{R_1} (V_1 - V_-)$ ideal op-amp $v_- = v_+$

$$= \left(1 + \frac{R_2}{R_1}\right) \frac{R_4}{R_3 + R_4} V_2 - \frac{R_2}{R_1} V_1$$

$$= \boxed{\frac{R_4 (R_1 + R_2)}{R_1 (R_3 + R_4)} V_2 - \frac{R_2}{R_1} V_1}$$

b. connecting a load resistor from V_0 to ground does not change V_0 since R_L would not show up in Kirchhoff current equations

c. $V_1 = V_2$, $R_1 = 1\text{ k}\Omega$, $R_2 = 30\text{ k}\Omega$, $R_3 = 1.5\text{ k}\Omega$

$$V_0 = 0 \rightarrow R_4 (R_1 + R_2) = R_2 (R_3 + R_4)$$

$$\boxed{R_4 = \frac{R_2 R_3}{R_1} = 45\text{ k}\Omega}$$


d. $V_2 = 0$, $V_1 = 1\text{ V}$ use previous resistor values

$$V_0 = -\frac{R_2}{R_1} V_1$$

$$= -30\text{ V} \rightarrow \text{power supply limits to } \pm 15\text{ V}$$

$$\boxed{V_0 = -15\text{ V}}$$

Ex 15.14)

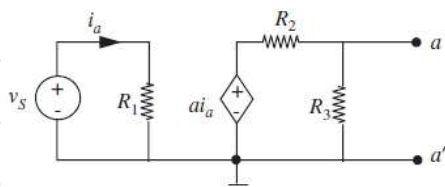

$$i_a = \frac{V_s}{R_1}$$


$$V' = a i_a = \frac{a V_s}{R_1}$$

$$\boxed{V_{TH} = \frac{R_3}{R_2 + R_3} V' = \frac{a R_3}{R_1 (R_2 + R_3)} V_s}$$

$$i_{sc} = \frac{V'}{R_2} \quad (\text{short output terminals})$$

$$\boxed{R_{TH} = \frac{V_{TH}}{i_{sc}} = \frac{R_2 R_3}{R_2 + R_3}}$$

Ex 15.16)

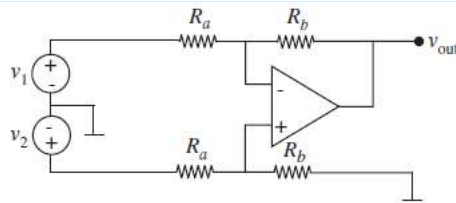

$$V_+ = V_2 \frac{R_b}{R_a + R_b} = V_-$$


$$\therefore \frac{V_1 - V_-}{R_a} = \frac{V_- - V_{out}}{R_b}$$

$$V_{out} = V_- \left(1 + \frac{R_b}{R_a}\right) - \frac{R_b}{R_a} V_1$$

$$= V_2 \frac{R_b}{R_a + R_b} \left(\frac{R_a + R_b}{R_a}\right) - \frac{R_b}{R_a} V_1$$

$$V_{out} = \frac{R_b}{R_a} (V_2 - V_1)$$

Ex 15.22)

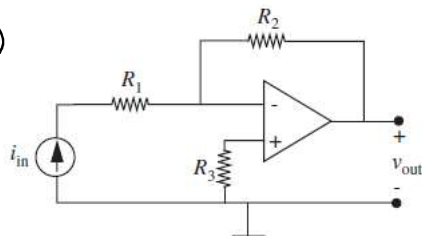


a. Ideal Op-Amp

$$V_+ = 0 = V_1$$

$$V_{out} = -i_{in} R_2$$

b.

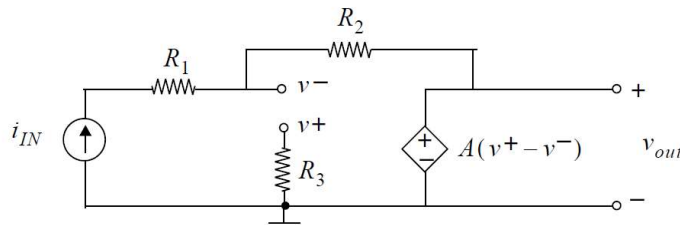


c. $v^+ = 0$

$$A(v^+ - v^-) - v^- = -i_{in} R_2$$

$$(A+1)v^- = i_{in} R_2 \rightarrow v^- = \frac{i_{in} R_2}{1+A}$$

$$V_{out} = -A v^- = -\frac{A i_{in} R_2}{1+A}$$

Pr 15.8)

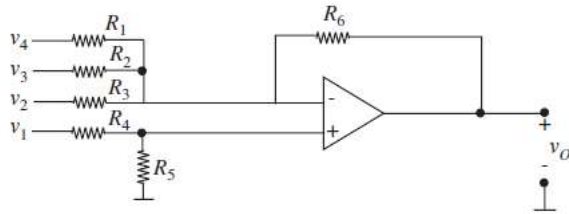

choose R s.t. $v_o = 2v_1 - 5v_2 - v_3 - 3v_4$

$$\frac{v_- - v_o}{R_6} = \frac{v_4 - v_-}{R_1} + \frac{v_3 - v_-}{R_2} + \frac{v_2 - v_-}{R_3}$$

$$v_- = v_+ = \frac{R_5}{R_4 + R_5} v_1$$

$$v_o = v_- \left(1 + \frac{R_6}{R_1} + \frac{R_6}{R_2} + \frac{R_6}{R_3} \right) - \frac{R_6}{R_1} v_4 - \frac{R_6}{R_2} v_3 - \frac{R_6}{R_3} v_2$$

$$= \frac{R_5}{R_4 + R_5} \left(1 + \frac{R_6}{R_1} + \frac{R_6}{R_2} + \frac{R_6}{R_3} \right) v_1 - \frac{R_6}{R_3} v_2 - \frac{R_6}{R_2} v_3 - \frac{R_6}{R_1} v_4$$

$$\frac{R_6}{R_3} = 5, \quad \frac{R_6}{R_2} = 1, \quad \frac{R_6}{R_1} = 3$$

$$\frac{R_5}{R_4 + R_5} = \frac{2}{10} = \frac{1}{5}$$