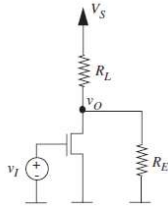


Homework 7

Wednesday, May 17, 2017 11:26 AM

Pr 7.14)



$$V_{GS} = V_I \quad V_{DS} = V_D = V_O$$


$$I_{ds} = \frac{I_{DSS}}{V_{GS(off)}^2} (V_{GS} - V_T)^2 \quad \frac{2I_{DSS}}{V_{GS(off)}^2} \equiv K$$

$$I_{ds} + \frac{V_O}{R_E} = \frac{V_S - V_O}{R_L}$$

$$\frac{K}{2} (V_I - V_T)^2 = \frac{V_S - V_O}{R_L} - \frac{V_O}{R_E} = \frac{V_S}{R_L} - \left(\frac{R_E + R_L}{R_E R_L} \right) V_O$$

$$V_O = \frac{R_E R_L}{R_E + R_L} \left(\frac{V_S}{R_L} - \frac{K}{2} (V_I - V_T)^2 \right)$$

Pr 7.15)

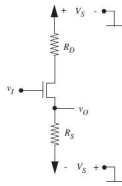

$$V_S = i_D R_D + V_{Fet} + i_D R_S - V_S$$

$$2V_S - i_D (R_S + R_D) = V_{Fet}$$

$$i_D = \frac{K}{2} (V_{GS} - V_T)^2 \quad V_{GS} = V_G - V_O = V_I - V_O \quad V_O = i_D R_S - V_S$$

$$= \frac{K}{2} (V_I - i_D R_S + V_S - V_T)^2$$

$$\frac{KR_S^2}{2} i_D^2 - (1 + KR_S (V_I + V_S - V_T)) i_D + \frac{K}{2} (V_I + V_S - V_T)^2 = 0$$

$$i_D = \frac{1}{KR_S^2} \left(KR_S (V_I + V_S - V_T) + 1 \pm \sqrt{(1 + KR_S (V_I + V_S - V_T))^2 - K^2 R_S^2 (V_I + V_S - V_T)^2} \right)$$

$$= \frac{1}{R_S} (V_I + V_S - V_T) + \frac{1}{KR_S^2} \pm \frac{1}{KR_S^2} \sqrt{2KR_S (V_I + V_S - V_T) + 1}$$


$$= \frac{1}{R_S} (V_I + V_S - V_T) + \frac{1}{KR_S^2} - \sqrt{\frac{2}{KR_S^3} (V_I + V_S - V_T) + \frac{1}{K^2 R_S^4}}$$

$$V_O = i_D R_S - V_S$$

$$= V_I - V_T + \frac{1}{KR_S} - \sqrt{\frac{2}{KR_S^3} (V_I + V_S - V_T) + \frac{1}{K^2 R_S^4}}$$

$$V_O (V_I = 0) = -V_T + \frac{1}{KR_S} - \sqrt{\frac{2}{KR_S^3} (V_S - V_T) + \frac{1}{K^2 R_S^4}}$$

Pr 7.16)

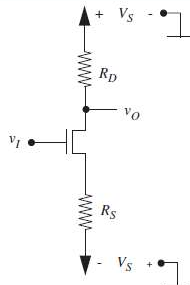

set-up is exactly the same as above, just moving \$V_O\$


$$V_O = V_S - i_{DS} R_D$$

$$i_{DS} = \frac{1}{R_S} (V_I + V_S - V_T) + \frac{1}{KR_S^2} - \sqrt{\frac{2}{KR_S^3} (V_I + V_S - V_T) + \frac{1}{K^2 R_S^4}}$$

$$V_O = V_S \left(1 - \frac{R_D}{R_S} \right) - \frac{R_D}{R_S} (V_I - V_T) - \frac{R_D}{KR_S^2} + R_D \sqrt{\frac{2}{KR_S^3} (V_I + V_S - V_T) + \frac{1}{K^2 R_S^4}}$$

$$V_O (V_I = 0) = V_S \left(1 - \frac{R_D}{R_S} \right) + \frac{R_D}{R_S} V_T - \frac{R_D}{KR_S^2} + R_D \sqrt{\frac{2}{KR_S^3} (V_S - V_T) + \frac{1}{K^2 R_S^4}}$$

Pr 7.17)

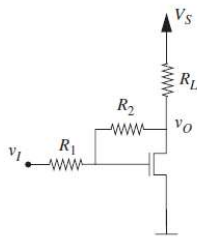

$$i_{DS} = \frac{K}{2} (V_{GS} - V_T)^2$$

$$V_{GS} = V_G = \frac{R_2}{R_1 + R_2} (V_I - V_O) + V_O$$

$$i_{DS} = \frac{V_S - V_O}{R_L} + \frac{V_I - V_O}{R_1 + R_2}$$

define $R_T = R_1 + R_2$

$$V_{GS} = \frac{R_2}{R_T} V_I + \frac{R_1}{R_T} V_O$$

$$i_{DS} = \frac{V_S - V_O}{R_L} + \frac{V_I - V_O}{R_T} = \frac{K}{2} \left(\frac{R_2}{R_T} V_I + \frac{R_1}{R_T} V_O - V_T \right)^2$$

$$\frac{V_S}{R_L} + \frac{V_I}{R_T} - \frac{R_L + R_T}{R_L R_T} V_O = \frac{K}{2} \left(\frac{R_1}{R_T} \right)^2 V_O^2 + \frac{K R_1}{R_T} V_O \left(\frac{R_2}{R_T} V_I - V_T \right) + \frac{K}{2} \left(\frac{R_2}{R_T} V_I - V_T \right)^2$$

$$0 = \frac{K}{2} \left(\frac{R_1}{R_T} \right)^2 V_O^2 + \left[\frac{K R_1}{R_T} \left(\frac{R_2}{R_T} V_I - V_T \right) + \frac{R_L + R_T}{R_L R_T} \right] V_O + \frac{K}{2} \left(\frac{R_2}{R_T} V_I - V_T \right)^2 - \frac{V_S}{R_L} - \frac{V_I}{R_T}$$