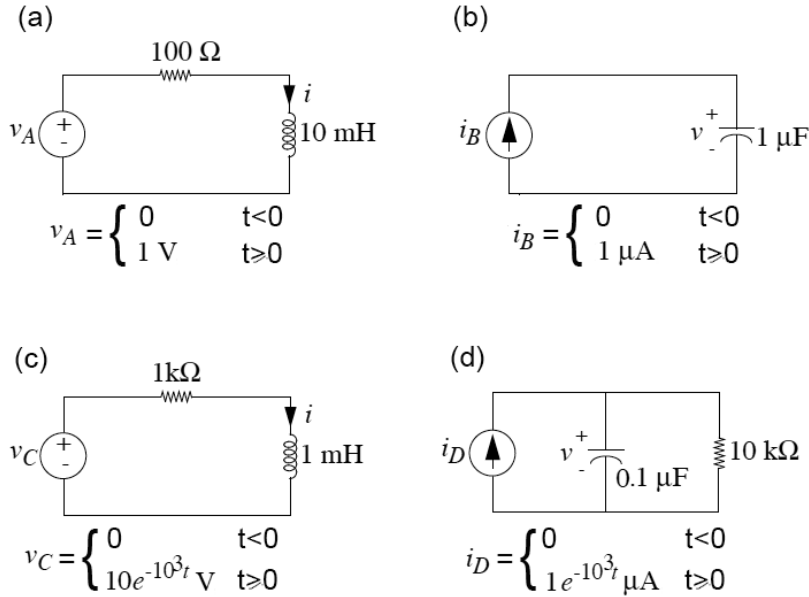


Final Exam for Physics 120A (closed book)
Thursday 12 June 2014; 8:00 - 11:00 AM

Problem 1.


For each of the circuits (a - d) below, find the indicated voltage (v) or current (i) for all $t > 0$. Time "t" is in seconds.



Problem 2.

The circuit below is called a differential amplifier.

- Using the ideal Op Amp model (infinite open loop gain, infinite input resistance, zero output resistance) derive an expression for the output voltage v_O in terms of the input voltages v_1 and v_2 and the resistances R_1 , R_2 , R_3 , and R_4 .
- Does connecting a load resistor R_L between the output and ground change the previous expression for v_O ? Why?
- Let $v_1 = v_2$ and $R_1 = 1 \text{ k}\Omega$, $R_2 = 30 \text{ k}\Omega$, and $R_3 = 1.5 \text{ k}\Omega$. Find R_4 so that $v_O = 0$.
- Let $v_2 = 0$ and $v_1 = 1 \text{ Volt}$. Using the preceding resistor values, including that computed for R_4 in part (c), find v_O .

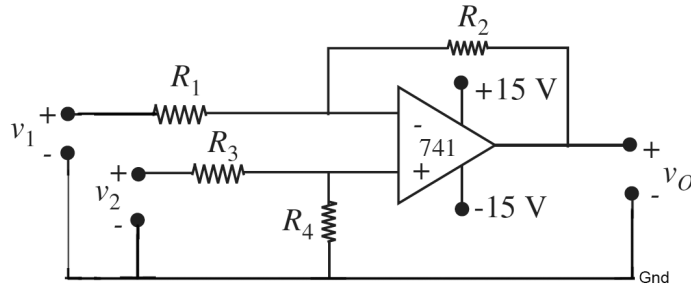


Problem 3.

(a) In the circuit below, assume that the diode can be modeled as an ideal diode. Plot the waveform $v_o(t)$ assuming a triangle wave input for $v_i(t)$.

(b) Write an expression for $v_o(t)$ in terms of $v_i(t)$ and R .

(c) If the triangle wave has a peak amplitude of only 2 Volts, a more accurate diode model must be used. Plot the waveform for $v_o(t)$ assuming that the diode is modeled using an ideal diode in series with a 0.6-Volt source.

(d) Write an expression for $v_o(t)$ in terms of $v_i(t)$ and R assuming that the diode is modeled using an ideal diode in series with a 0.6-Volt source.

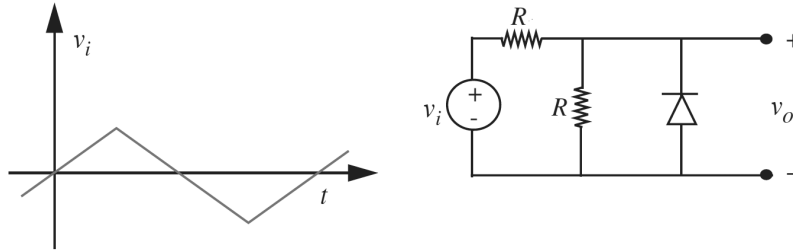


Problem 4.

Consider the common emitter BJT amplifier shown below. The input voltage comprises the sum of a DC bias voltage, $V_I = 0.7$ Volts, and a sinusoid of the form $v_i(t) = 0.001 \sin(\omega t)$ Volts.

In your analysis of the circuit, you may assume that the amplitude of $v_i(t)$ is very small compared to V_I , and that the BJT always operates in its active region. The figure also shows a small-signal model for the BJT in its active region.

Let the output voltage comprise an operating-point voltage V_O and a small-signal response term $v_o(t)$.

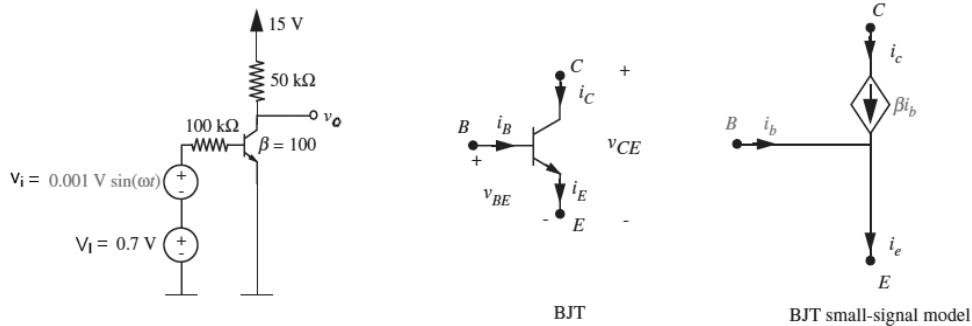- (a) Determine the operating-point voltage V_O for the input bias of $V_I = 0.7$ Volts.
- (b) Draw the small-signal equivalent circuit for the amplifier?
- (c) Determine the small-signal gain of the amplifier?
- (d) What is the small-signal response $v_o(t)$ given the small signal input $v_i(t)$?



Fini!