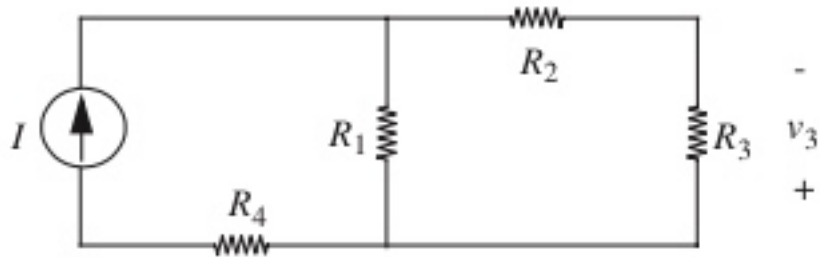


# PHYS120 SPRING 2015 FINAL EXAM

Please read all directions carefully and be sure to solve for only what is asked.  
Professor David Kleinfeld

## Problem 1

Determine explicitly the voltage  $v_3$  in the following circuit:



## Problem 2

- Assuming the diode can be modeled as an ideal diode, and  $R_1 = R_2$ , plot the waveform  $v_o(t)$  for the circuit in Figure 4.57, assuming a triangle wave input. Write an expression for  $v_o(t)$  in terms of  $v_i$ ,  $R_1$ , and  $R_2$ .
- If the triangle wave has a peak amplitude of only 5 volts, and  $R_1 = R_2$ , a more accurate diode model must be used. Plot and write an expression for  $v_o$  assuming that the diode is modeled using an ideal diode in series with a 0.6-volt source. Draw the transfer curve  $v_o$  versus  $v_i$ .


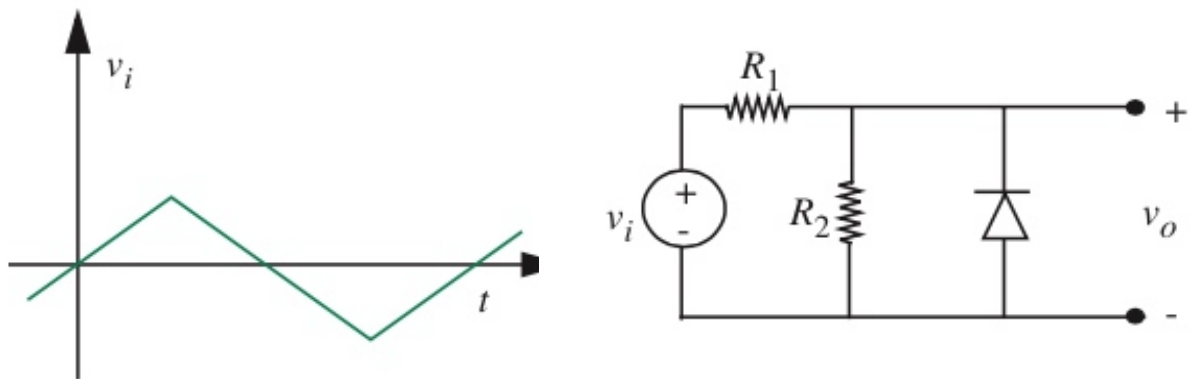


FIGURE 4.57


### Problem 3

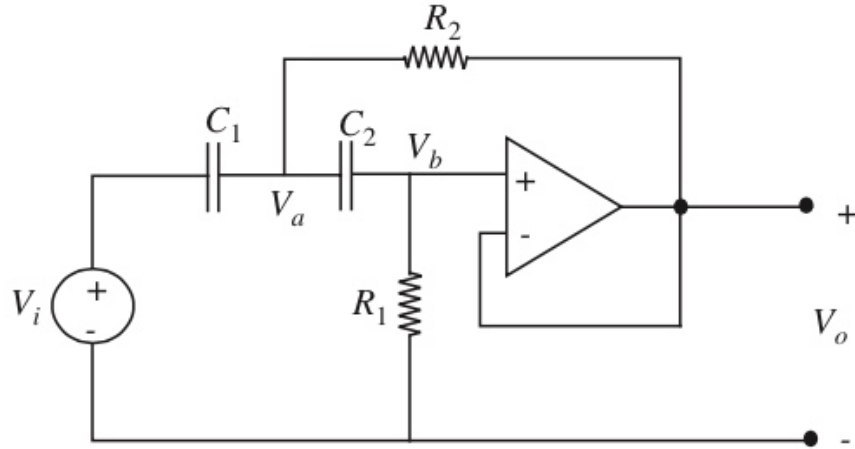

- Write the sinusoidal steady state node equations for the complex amplitudes of  $V_a$  and  $V_b$ .
- Solve for  $V_o/V_i$  using the results in (a). Simplify your answer so that the denominator follows the form  $As^2 + Bs + C$ . This will help you in the next step.
- Assuming the circuit is under-damped, find the frequency at which the peak occurs, the magnitude of the transfer function at the peak, and the  $Q$  of resonance.

\*YOU DO NOT NEED TO GRAPH THIS.


### Problem 4

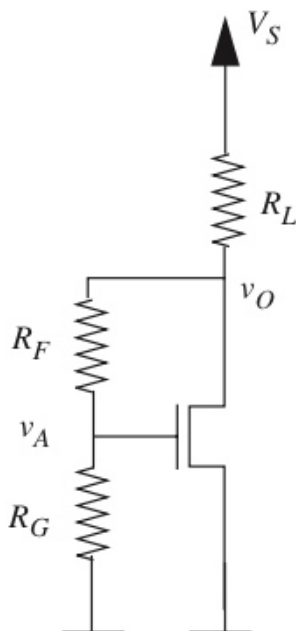

Consider the MOSFET circuit shown to the left. Determine the value of  $V_O$  in terms of the other circuit parameters. Assume the MOSFET is in saturation and is characterized by the parameters  $K$  and  $V_T$ .

HINT:  $V_A$  should NOT be in your answer.

### Problem 5

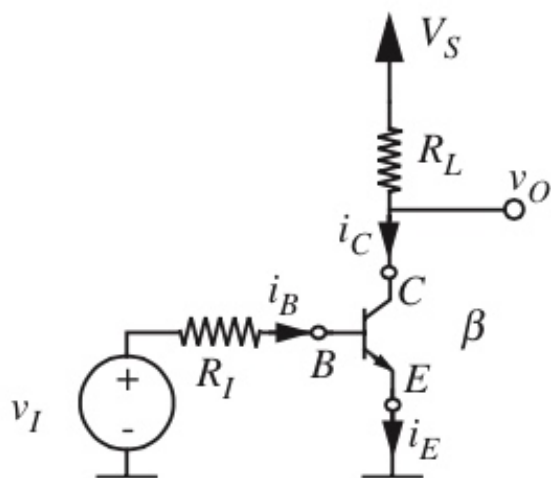

Consider the BJT amplifier to the left. Assume that the BJT is characterized by the large signal model and that the BJT operates in its active region. Assume further that  $V_S = 10\text{ V}$ ,  $R_L = 20\text{ k}\Omega$ ,  $R_I = 500\text{ k}\Omega$  and  $\beta = 100$ .

- Write an expression relating  $V_O$  to  $i_C$
- Write an expression relating  $i_C$  to  $V_I$
- Write an expression relating  $i_E$  to  $i_B$
- Write an expression relating  $V_O$  to  $V_I$
- What is the value of  $V_O$  for an input voltage  $V_I = 1$ ? What are the corresponding values of  $i_B$ ,  $i_C$ , and  $i_E$

### Problem 6

$$(A + \bar{B})(\bar{A} \cdot \bar{B} + C) + \overline{C \cdot D}$$

$$(A \cdot \bar{C} + \bar{B} \cdot D)(\overline{D + \bar{B} + A})$$

$$A + \overline{\bar{B} \cdot D} + A \cdot C \cdot \bar{D}$$

$$\overline{((A + \bar{C}) + B + \bar{D}) + A \cdot \bar{C} \cdot D}$$

- Give an implementation using gates for each of the four logic expressions.
- Write the truth table for each of the four expressions.
- Suppose you know that  $A = 0$ . Simplify the four expressions under this constraint.
- Simplify the four expressions assuming that  $A$  and  $B$  are related as  $A = \bar{B}$ .

\*\*\*THE END\*\*\*

\* If you so choose, draw a picture of Dr. Kleinfeld in the space you have remaining in your blue book.

\*Best one gets +1 point to their final!