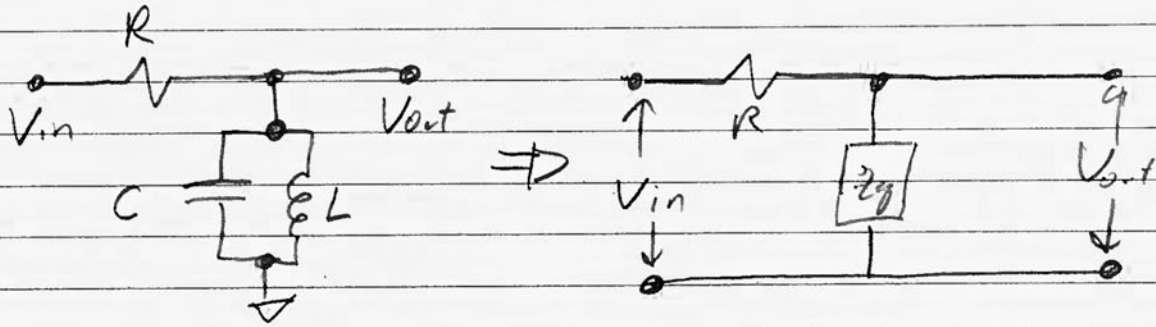


Notes on circuit 3.1 in laboratory #3 - Physics 120



$$\frac{V_{out}}{V_{in}} = \frac{Z_{eq}}{R + Z_{eq}} ; \text{ but } Z_{eq} = \frac{\frac{1}{j\omega C} j\omega L}{\frac{1}{j\omega C} + j\omega L}$$

$$= \frac{j\omega L}{1 - \omega^2 LC}$$

$$= R \frac{j\omega \tau}{1 - (\omega/\omega_0)^2}$$

where $\tau = L/R$; $\omega_0 = 1/\sqrt{LC}$

$$= \frac{j\omega \tau}{1 - (\omega/\omega_0)^2} \cdot \frac{1}{1 + j\omega \tau / [1 - (\omega/\omega_0)^2]}$$

$$= \frac{j\omega \tau}{[1 - (\omega/\omega_0)^2] + j\omega \tau}$$

$$= \frac{j\omega \tau \{ [1 - (\omega/\omega_0)^2] - j\omega \tau \}}{[1 - (\omega/\omega_0)^2]^2 + (\omega \tau)^2}$$

$$= \omega \tau \frac{\omega \tau + j [1 - (\omega/\omega_0)^2]}{(\omega \tau)^2 + [1 - (\omega/\omega_0)^2]^2}$$

$$\left| \frac{V_{out}(\omega)}{V_{in}(\omega)} \right| = \frac{\omega \tau}{\sqrt{(\omega \tau)^2 + [1 - (\omega/\omega_0)^2]^2}}$$