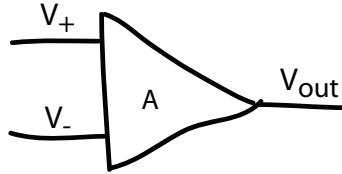


## Notes on Op Amp Configurations; Physics 120: David Kleinfeld, Spring 2017

An Operation Amplifier is constructed from circuit elements - transistors, etc. - yet may be considered as a functional device that takes the difference of two-signals and produces an output that is a high-gain version of this difference.




In the idealized case:

- The output is  $V_{out} = A(V_+ - V_-)$  with the open-loop gain,  $A$ , tending to infinity (easily  $10^6$  in practice).
- The inputs have infinite impedance (as much as  $10^{12} \Omega$  in practice).
- The output has zero impedance (as low as  $10 \Omega$  in practice).


The Operation Amplifier is an active device that require an external power source; in our analysis we have left out the power leads (typically both +15 V and -15 V, each taken relative to the same common as used for the inputs and output).

### Case 1. Non-inverting buffer

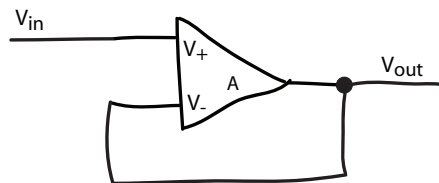

We have  $V_{out} = A(V_+ - V_{out})$  or  $V_{out} = \frac{A}{A+1}V_+$  or  $V_{out} \xrightarrow{A \rightarrow \infty} V_+$ . The gain is  $G = \frac{A}{A+1} \xrightarrow{A \rightarrow \infty} 1$

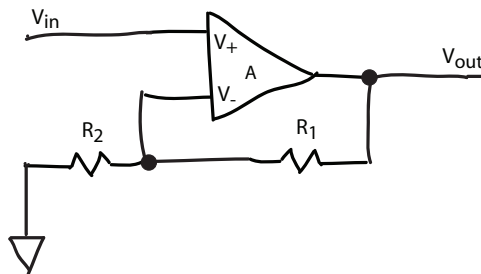
### Case 2. Non-inverting buffer with gain (used in extracellular/intracellular amps)



Only a fraction of the output voltage,  $V_- = \frac{R_2}{R_1 + R_2}V_{out}$ , is sensed. This forces the output voltage

to be proportionally greater, so have  $V_{out} \xrightarrow{A \rightarrow \infty} \left(1 + \frac{R_1}{R_2}\right)V_+$ . The gain is  $G \xrightarrow{A \rightarrow \infty} 1 + \frac{R_1}{R_2}$ .

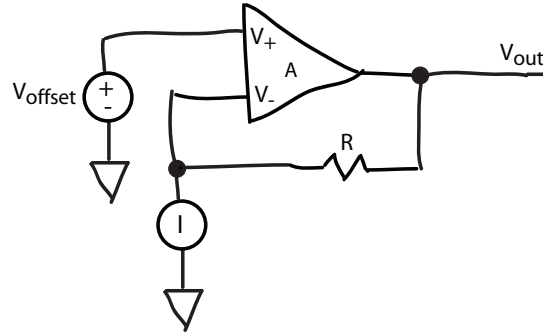
**Case 3. Current-to-voltage converter (used as photodiode/photomultiplier tube amplifiers)**



We have the node equation  $\frac{(V_- - V_{out})}{R} = I$  as well as  $V_{out} = A(V_+ - V_-)$ , so that  $V_{out} = \frac{A}{A+1}(V_+ - IR)$  or  $V_{out} \xrightarrow{A \rightarrow \infty} V_+ - IR$ . The input  $V_+$  is either grounded or set to an offset voltage  $V_{offset}$ .

It is instructive to calculate the input impedance seen by the current source  $I$ . We take  $V_+ = 0$  for simplicity and find the impedance is  $R_{in} = \frac{V_-}{I} = \frac{R}{1+A}$ . Thus as the open-loop gain,  $A$ , goes to infinity, the input to the current measurement goes to zero.

**Case 4. Summing amplifier with gain.**

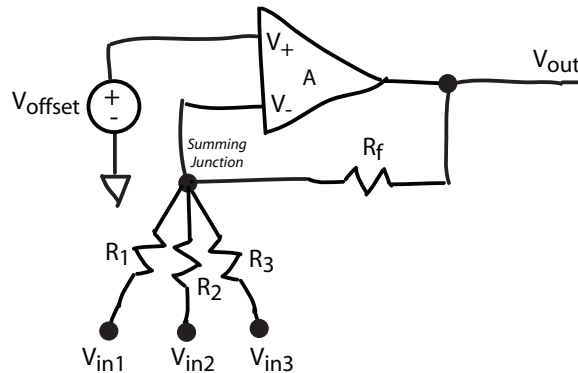

Here we convert input voltages into input currents by passing them through a resistor, and sum these currents with the above circuit. The summing junction makes use of the effective low input impedance to the current-to-voltage converter,  $R_{in} \approx R_f/A$ . The current from input voltage  $V_1$  is  $V_1/R_1$ , that from  $V_2$  is  $V_2/R_2$ , etc. These currents sum so that  $V_{out} \xrightarrow{A \rightarrow \infty} V_+ - R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$ .

The gain per input channel "i" is just  $G_i \xrightarrow{A \rightarrow \infty} -\frac{R_f}{R_i}$ .