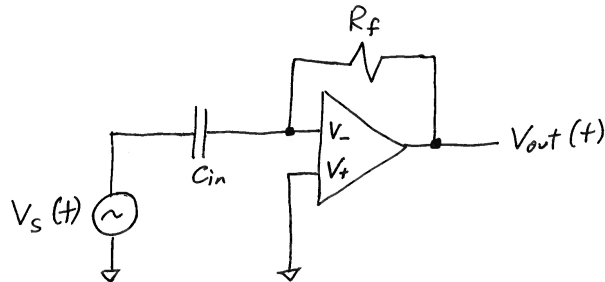


Notes on an Op Amp Differentiator Circuit; Physics 120: David Kleinfeld, Spring 2017

An operation amplifier may be configured as a differentiator, AKA a high pass filter, using a capacitor as the source impedance and a resistor as the feedback impedance in an inverting amplifier configuration.



The above circuit can be analyzed in the time domain as:

$$0 = C_{in} \frac{d[V_-(t) - V_s(t)]}{dt} + \frac{V_-(t) - V_{Out}(t)}{R_f}$$


$$V_{Out}(t) = A [V_+(t) - V_-(t)]$$

$$V_+(t) = 0$$

and for $A \rightarrow \infty$ yields:

$$V_{Out}(t) = -R_f C_{in} \frac{d[V_s(t)]}{dt}$$

In the frequency domain we have

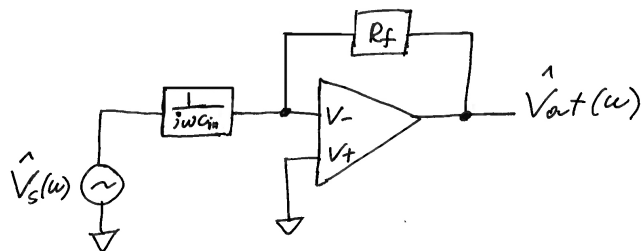


and


$$\hat{V}_{Out}(\omega) = -\frac{R_f}{1/j\omega C_{in}} \hat{V}_s(\omega) = -i\omega R_f C_{in} \hat{V}_s(\omega)$$

This is an ideal differentiator. One problem is that the closed loop gain $|G(\omega)| = \omega R_f C_s$ grows, even as the frequency approaches the value where the open loop gain $A(\omega)$ experiences large phase shifts that lead to positive feedback with associated distortion and saturation of the output. We thus need to "roll-off" the closed loop gain at high frequencies so that it varies as $|G(\omega)| \propto 1/\omega$ rather than as $|G(\omega)| \propto \omega$.

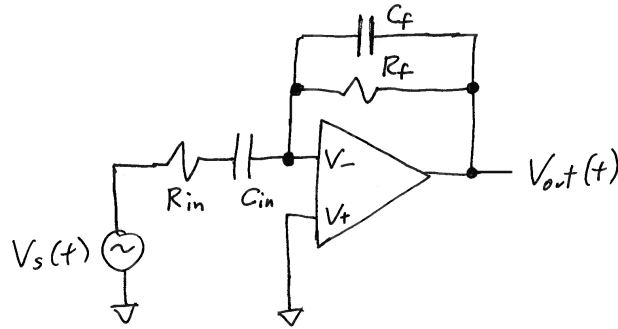We add a resistor in series with the input so that the gain will saturate at high frequencies. We add a capacitor in parallel with the feedback so that the output will further turn integrative at high frequencies. The new circuit looks like:



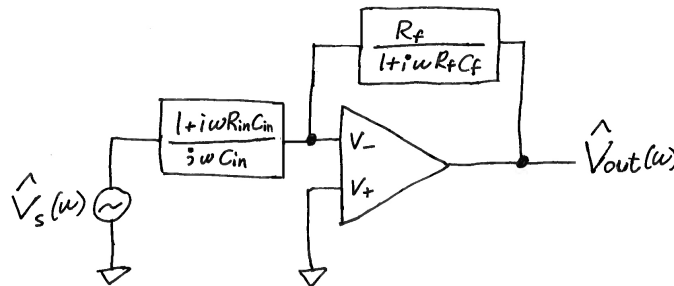In the frequency domain, the combined components yield a circuit with both complex source and feedback impedances:



Thus

$$\hat{V}_{out}(\omega) = -\frac{R_f}{1 + i\omega R_f C_f} \times \frac{i\omega C_{in}}{1 + i\omega R_{in} C_{in}} \hat{V}_s(\omega) = \dots = -i\omega R_f C_{in} \frac{1 - \omega^2 R_f C_f R_{in} C_{in} - i\omega(R_f C_f + R_{in} C_{in})}{[1 + (\omega R_f C_f)^2][1 + (\omega R_{in} C_{in})^2]} \hat{V}_s(\omega)$$

The magnitude of the closed loop gain is just:

$$|G(\omega)| = \left| \frac{\hat{V}_{out}(\omega)}{\hat{V}_s(\omega)} \right| = \frac{\omega R_f C_{in}}{\sqrt{[1 + (\omega R_f C_f)^2][1 + (\omega R_{in} C_{in})^2]}}$$

and clearly has the desired fall-off properties with increasing frequency.

FOR HOMEWORK:

- (1) Draw a Bode magnitude plot, $\log |G(\omega)|$ versus $\log \omega$, with $1 \gg R_{in} C_{in} \gg R_f C_f$. Identity the break points, the slope in each portion of the plot, e.g., $d|G(\omega)|/d\omega = \omega R_f C_{in}$ for limiting case of $\omega \rightarrow 0$, and the maximum gain.
- (2) Write an expression for the phase of $G(\omega)$ as a function of ω .
- (3) Draw a Bode phase plot, $\text{phase}\{G(\omega)\}$ versus $\log \omega$, with $1 \gg R_{in} C_{in} \gg R_f C_f$. Identity the breaks and the asymptotic value of the phase. Compare with the value for the "ideal" differentiator.