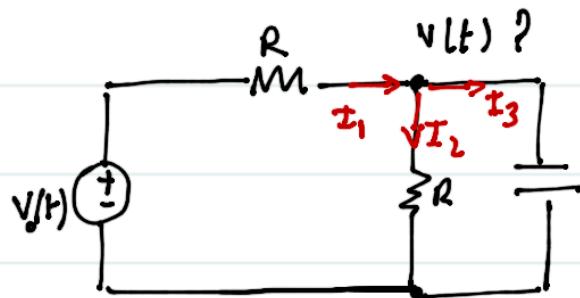


Phys 178/278 Homework #1 solutions

Question #1 - Circuits

a)



$$V_o(t) = \begin{cases} 0 & t < 0 \\ V_o & t \geq 0 \end{cases}$$

$$V(t) = \frac{Q_3}{C}$$

From Kirchoff's laws:

$$\textcircled{1} \quad I_1 = I_2 + I_3$$

$$\textcircled{2} \quad V_o(t) - I_1 R - I_2 R = 0$$

$$\textcircled{3} \quad \frac{Q_3}{C} - I_2 R = 0$$

Substituting into \textcircled{2}

$$V_o(t) - I_1 R - \frac{Q_3}{C} = 0$$

From \textcircled{1}

$$V_o(t) - (I_2 + I_3) R - \frac{Q_3}{C} = 0$$

$$V_o(t) - 2 \frac{Q_3}{C} - I_3 R = 0$$

$$I_3(t) = -2 \frac{Q_3}{RC} + \frac{V_o(t)}{R}$$

need to solve

$$\frac{dQ_3}{dt} = -\frac{2Q_3}{RC} + \frac{V_0(t)}{R}$$


$$Q_3(t) = \frac{V_0 C}{2} \left(1 - e^{-\frac{2}{RC} t}\right)$$

$$\Rightarrow V(t) = \frac{V_0}{2} \left(1 - e^{-\frac{2}{RC} t}\right)$$

Check whether limits make sense.

$$V(t=0) = 0 \quad \checkmark$$
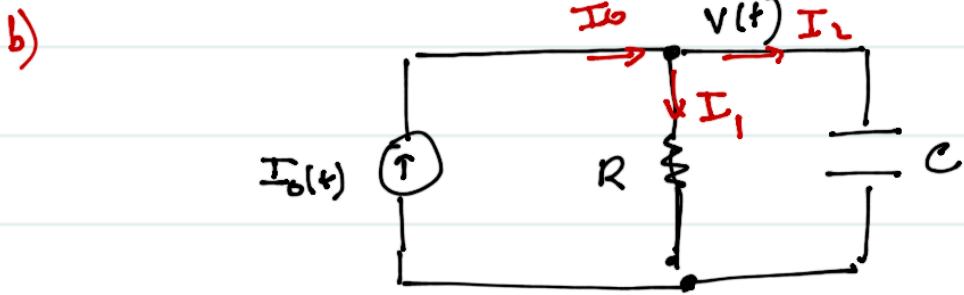
$$V(t \rightarrow \infty) = \frac{V_0}{2} \quad \checkmark$$



$$I_0(t) = \begin{cases} 0 & t < 0 \\ I_0 & 0 \leq t < a \\ 0 & t \geq a \end{cases}$$

For $t < 0$ $I_0 = 0$

$$V(t) = I_0 R = 0$$

For $0 \leq t < a$

$$\textcircled{1} \quad I_0 = I_1 + I_2$$

$$\textcircled{2} \quad I_1 R - \frac{Q_2}{C} = 0$$

$$\textcircled{2} \rightarrow \textcircled{1} \quad I_0 = \frac{Q_2}{RC} + I_2$$

$$\frac{dQ_2}{dt} = I_0 - \frac{Q_2}{RC}$$

$$Q_2(t) = I_0 RC (1 - e^{-t/RC})$$

$$V(t) = I_0 R (1 - e^{-t/RC})$$

For $t \geq a$

$$\textcircled{1} \quad I_1 = -I_2$$

$$\textcircled{2} \quad I_1 R - \frac{Q_2}{C} = 0$$

$$I_2 = -\frac{Q_2}{RC}$$

$$\cdot \frac{dQ_2}{dt} = -\frac{Q_2}{RC}$$

$$Q_2(t) = Q_2(a) e^{-(t-a)/RC}$$


$$v(t) = \frac{Q_2(a)}{C} e^{-(t-a)/RC}$$

$$v(t) = \frac{C}{I_0 R} (1 - e^{-a/RC}) e^{-(t-a)/RC}$$

$$v(t) = \begin{cases} 0 & t < 0 \\ I_0 R (1 - e^{-t/RC}) & 0 \leq t < a \\ I_0 R (1 - e^{-a/RC}) e^{-(t-a)/RC} & t \geq a \end{cases}$$

$v(t)$ is continuous at $t=0$ and $t=a$ ✓

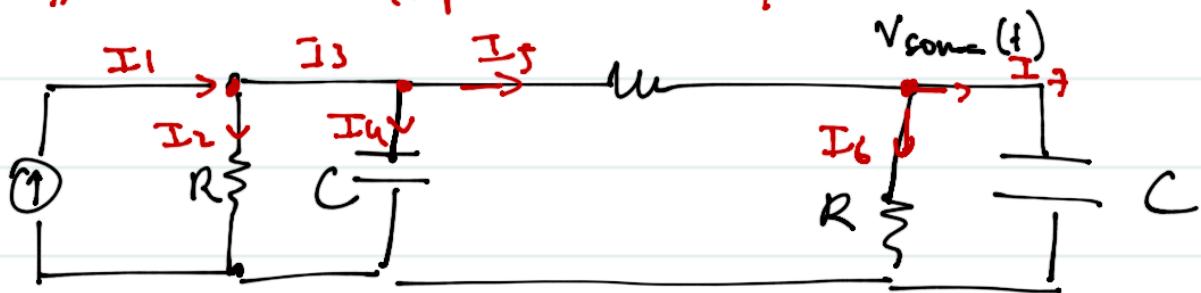Question # Circuit representation of a neuron



KCL:

$$\textcircled{1} \quad I_1 = I_2 + I_3$$

..

$$\textcircled{2} \quad I_3 = I_4 + I_5$$

$$\textcircled{3} \quad I_5 = I_6 + I_7$$

KVL:

$$\textcircled{4} \quad I_{2n} R = I_2 R .$$

$$\textcircled{5} \quad I_2 R - \frac{Q_u}{C} = 0$$

$$\textcircled{6} \quad \frac{Q_u}{C} - I_5 R + I_6 R = 0$$

$$\textcircled{7} \quad I_6 R - \frac{Q_7}{C} = 0$$

$$\textcircled{6} \rightarrow \textcircled{7} \quad \frac{Q_u}{C} - I_S R = \frac{Q_f}{C}$$

$$\textcircled{5} \rightarrow I_2 R - I_S R = \frac{Q_f}{C}.$$

$$\textcircled{4} \rightarrow I_{Syn} R - I_S R = \frac{Q_f}{C}$$

$$\textcircled{3} \rightarrow I_{Syn} R - (I_6 + I_7) R = \frac{Q_f}{C}$$

$$I_{Syn} R - I_7 R = \frac{2 Q_f}{C}$$

For $t < 0$

$$\frac{dQ_f}{dt} = -\frac{2Q_f}{RC}$$

$$\tau = RC.$$

$$Q_f(t) = Q_0 e^{-2t/\tau}$$

$$Q_f(t=0) = 0 \Rightarrow Q_0 = 0.$$

For $0 < t < a$

$$I_o R - \frac{dQ_f}{dt} R = \frac{2Q_f}{C}$$

$$\frac{dQ_f}{dt} = I_o - \frac{2Q_f}{RC}.$$

$$Q_7(t) = I_0 R C \left(1 - e^{-\frac{t}{RC}}\right)$$

$$Q_7(t=0) = 0 \checkmark$$

$$Q_7(t=a) = I_0 R C \left(1 - e^{-\frac{2a}{RC}}\right)$$

For $t > a$.


$$\frac{dQ_7}{dt} = -\frac{2Q_7}{RC}$$

$$Q_7(t) = Q_7(t=a) e^{-\frac{2(t-a)}{RC}}$$

$$Q_7(t) = I_0 R C \left(1 - e^{-\frac{2a}{RC}}\right) e^{-\frac{2(t-a)}{RC}}$$

$$V_{\text{some}}(t) = \begin{cases} 0 & t < a \\ I_0 R \left(1 - e^{-\frac{2t}{RC}}\right) & 0 \leq t < a \\ I_0 R \left(1 - e^{-\frac{2a}{RC}}\right) e^{-\frac{2(t-a)}{RC}} & t \geq a \end{cases}$$

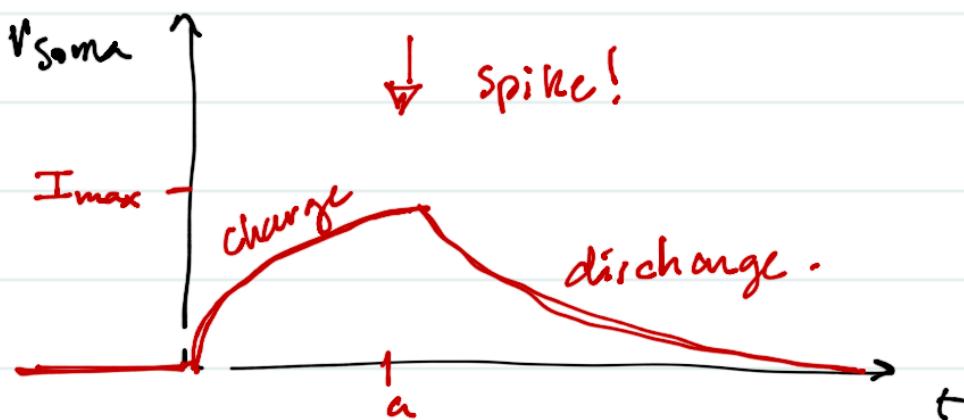$\underbrace{I_0 R \left(1 - e^{-\frac{2a}{RC}}\right)}_{I_{\max}}$



Question #4 Two binary neurons w/ mutual inhibition

$$s_i^{t+1} = \begin{cases} 1 & w_i s_i^t > \theta_2 \\ -1 & w_i s_i^t < \theta_2 \\ s_i^t & w_i s_i^t = \theta_2 \end{cases}$$

a) s_i^t is a fixed point $\Leftrightarrow s_i^{t+1} = s_i^t$
 $s_i^t = (+1, +1)$

$$\begin{aligned} s_1^{t+1} &= \operatorname{sgn}(w_2 s_2^t - \theta_1) \\ &= \operatorname{sgn}(w_2 - \theta_1) \end{aligned}$$

$$\begin{aligned} s_2^{t+1} &= \operatorname{sgn}(w_1 s_1^t - \theta_2) \\ &= \operatorname{sgn}(w_1 - \theta_2) \end{aligned}$$

$$s^{t+1} = \begin{pmatrix} \operatorname{sgn}(w_2 - \theta_1) \\ \operatorname{sgn}(w_1 - \theta_2) \end{pmatrix} = \begin{pmatrix} +1 \\ +1 \end{pmatrix}$$

$$\Rightarrow w_2 > \theta_1 \quad \text{and} \quad w_1 > \theta_2 \quad \text{---}$$

$$\begin{aligned} s^t &= (+1, -1) \\ s^{t+1} &= \begin{pmatrix} \operatorname{sgn}(-w_2 - \theta_2) \\ \operatorname{sgn}(w_1 - \theta_2) \end{pmatrix} = \begin{pmatrix} +1 \\ -1 \end{pmatrix} \end{aligned}$$

$$\Rightarrow -w_2 > \theta_1 \quad \text{and} \quad \theta_2 > +w_1$$

• $s^t = (-1, +1)$

$$s^{t+1} = \begin{pmatrix} \operatorname{sgn}(+w_2 - \theta_1) \\ \operatorname{sgn}(-w_1 - \theta_2) \end{pmatrix} = \begin{pmatrix} -1 \\ +1 \end{pmatrix}$$


$$\Rightarrow \theta_1 > +w_2 \quad \text{and} \quad -w_1 > \theta_2$$

• $s^t = (-1, -1)$

$$s^{t+1} = \begin{pmatrix} \operatorname{sgn}(-w_2 - \theta_3) \\ \operatorname{sgn}(-w_1 - \theta_2) \end{pmatrix} = \begin{pmatrix} -1 \\ -1 \end{pmatrix}$$

$$\Rightarrow \theta_1 > -w_2 \quad \text{and} \quad \theta_2 > -w_1$$

2- Recall $w_1, w_2 < 0$

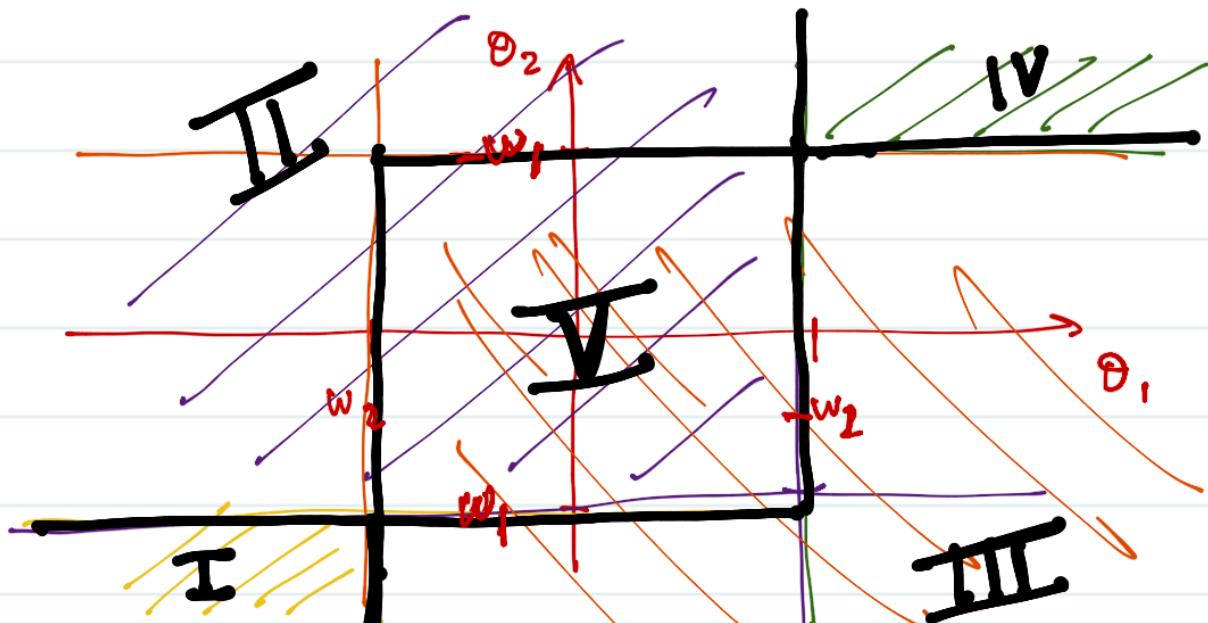

Question #5 Binary neurons w/ symmetric connection

1- $\Delta E = -(\mu_i - \theta_i) \Delta s_i$

where $\mu_i = \sum_{j=1, j \neq i} w_{ij} s_j + I_{j, \text{ext}}$

and $\Delta s_i = s_i^{t+1} - s_i^t$

Case 1: $\Delta E = 0 \Leftrightarrow \mu_i = \theta_i$ or $\Delta s_i = 0$

. if $\mu_i = \theta_i$, then $s_i^{t+1} = s_i^t$

so there is no change in s_i

. if $\Delta s_i = 0$, then $s_i^{t+1} = s_i^t$

so there is no change in s_i

therefore $\Delta E = 0 \Leftrightarrow$ no change in neuron state

Case 2: $\Delta E < 0 \Leftrightarrow (\mu_i - \theta_i) \Delta s_i > 0$

. $\mu_i > \theta_i$ and $\Delta s_i > 0$

if $\mu_i > \theta_i$ then $s_i^{t+1} = +1$

since $\Delta s_i = s_i^{t+1} - s_i^t > 0$

then $s_i^t = -1$

the state of the neuron flips

• $\mu_i < \theta_i$ and $\Delta s_i < 0$

if $\mu_i < \theta_i$ then $s_i^{t+1} = -1$

since $\Delta s_i = s_i^{t+1} - s_i^t < 0$

then $s_i^t = +1$

the state of the neuron flips.

therefore the state of the neuron flips $\Leftrightarrow \Delta E < 0$

2. Direction 1 : Fixed point \rightarrow local min.

\vec{s} is a fixed point $\Leftrightarrow \Delta S = 0$, $s_i^{t+1} = s_i^t$

From part a) Case ① we've shown that $\Delta E = 0 \Leftrightarrow \Delta S = 0$

Suppose we flip the neuron $s_i^{t+1} = -s_i^t$ and get a local minimum $\Delta E \geq 0$. By part 1 Case ② we've shown that $\Delta E < 0$. this case is therefore not possible.

therefore if s_i^t is a fixed point it's also a local min.

Direction 2: local min \rightarrow fixed point.

A state is a local min if $\Delta E \geq 0 \quad \forall i: s_i^t \rightarrow -s_i^t$

But we've shown from part a) that if a neuron flips, $\Delta E < 0$ therefore s_i^t cannot flip for $\Delta E \geq 0$ and s_i^t is a fixed point.

3. From part a) we've shown that any update $\rightarrow \Delta E < 0$ and from part b) if \vec{s} is a fixed point it's also a local minima

$$S_1 \rightarrow S_2 \rightarrow S_3 \rightarrow \dots \rightarrow S^t$$

$$E_1 \geq E_2 \geq E_3 \dots \geq E^t$$

Since the number of states is finite $\exists E_j = \min \{E_i\}$

Since $\Delta E \leq 0$ $\Delta E_j = 0$

We've shown that if $\Delta E = 0$ the states do not flip and $\Delta S = 0$

therefore the system always reaches a fixed point at $t \rightarrow \infty$ if the number of states is finite

