

## Quiz 5

1.  $\circ V_{Na} - IR_{Na} - IR_{Leak} - V_{Leak} = 0$  (Kirchoff's loop rule)

$\circ V_{membrane} = V_{Na} - IR_{Na}$

$\frac{V_{Na} - V_{Leak}}{R_{Na} + R_{Leak}} = I$

Substituting,

$$V_{membrane} = V_{Na} - \left( \frac{V_{Na} - V_{Leak}}{R_{Na} + R_{Leak}} \right) R_{Na} = \frac{V_{Na} R_{Leak} + V_{Leak} R_{Na}}{R_{Na} + R_{Leak}}$$

2. (Brackets mean "the units of")

$$\Phi_B = B_{\perp} A$$

$$[\Phi_B] = [B_{\perp}] [A]$$

$$1 \text{ Wb} = 1 \text{ T} \cdot \text{m}^2$$

$$[B] = \frac{[F]}{[I][l]}$$

$$1 \text{ T} = 1 \text{ N/A} \cdot \text{m}$$

$$= 1 \frac{\text{kg} \cdot \text{m}}{\text{s}^2} \cdot \frac{1}{\text{A} \cdot \text{m}}$$

$$\therefore 1 \text{ Wb} = 1 \frac{\text{kg}}{\text{C} \cdot \text{s}} \cdot \text{m}^2$$

3.  $|\mathcal{E}| = N \frac{|\Delta \Phi_B|}{\Delta t}$

$|\Delta \Phi_B| = |\Delta B_{\perp}| A$  since  $A$  is constant

$$|\mathcal{E}| = NA \frac{|\Delta B_{\perp}|}{\Delta t}$$

$$= 10 [\pi (10 \times 10^{-6} \text{ m})^2] (1.0 \times 10^{-2} \text{ T/s})$$

$$|\mathcal{E}| = 3.1 \times 10^{-11} \text{ V}$$

## Quiz 5

$$4. \Delta \Phi_B = \Delta (B_{\perp} A) \\ = (\Delta B_{\perp}) A$$

because the loop's area is constant

▣ The magnetic flux through (into) the paper increases as the field strength increases, so a current is induced in the coil to create a flux in the opposite direction. To create a magnetic field out of the page (and therefore a flux because the wire initially caused no magnetic field), the current in the wire flows counterclockwise.

5. The current through an LR circuit at time  $t$  is given by

$$I = \frac{\mathcal{E}}{R} (1 - e^{-t/\tau})$$

When  $t=0$ ,  $e^{-t/\tau} = 1$ , so  $I = 0$

## Quiz 5

6. A long time after the switch is closed, the current is no longer changing, so  $\frac{\Delta I}{\Delta t} = 0$ . The voltage drop across an inductor is  $\mathcal{E} = -L \frac{\Delta I}{\Delta t}$ . Therefore, after a very long time, there is no voltage drop across the inductors. The voltage across the resistor equals the battery's voltage, so using Ohm's law,  $I = V/R$ .

7. Writing out the loop equation for the circuit,

$$V - L_1 \frac{\Delta I}{\Delta t} - L_2 \frac{\Delta I}{\Delta t} - IR = 0, \quad \text{we}$$

can combine terms:

$$V - (L_1 + L_2) \frac{\Delta I}{\Delta t} - IR = 0$$

Thus, the effect of two inductors in series is the same as one inductor whose inductance is the sum of the original inductors.

$$\therefore \tau = L/R \rightarrow \tau = \frac{L_1 + L_2}{R}$$

$$\tau = \frac{15 \times 10^{-6} \text{ H}}{8 \text{ } \Omega}$$

$$\tau = 1.9 \times 10^{-6} \text{ s}$$

## Quiz 5

$$8. \sum \vec{F} = -mg + I \vec{w} B$$

$I = \mathcal{E}/R$  where  $\mathcal{E}$  is the magnitude of the induced emf

$$\mathcal{E} = N \frac{\Delta \Phi_B}{\Delta t}$$

$$= N \frac{Bw(\Delta d)}{w(\Delta t)} \quad (N=1)$$

If  $a=0$ ,  $F=0$ , and the loop will move with constant (terminal) velocity.

$$v = \frac{\Delta d}{\Delta t} \quad \text{Substituting,}$$

$$-mg + \frac{Bwv}{R} B = 0$$

$$v = \frac{mgR}{(wB)^2}$$

# Quiz 5

$$10. B = \mu_0 n I$$

$$= (4\pi \times 10^{-7} \text{ T}\cdot\text{m/A}) \left( \frac{1000 \text{ turns}}{100 \times 10^{-2} \text{ m}} \right) (2.5 \text{ A})$$

$$B = 3.1 \times 10^{-3} \text{ T}$$

$$\Phi_B = B_{\perp} A$$

$$= (3.1 \times 10^{-3} \text{ T}) [\pi (5.0 \times 10^{-2} \text{ m})^2]$$

$$= 2.5 \times 10^{-5} \text{ Wb}$$

9.

$$\mathcal{E}_{\text{Max}} = NBA\omega$$

$$= (1000) (0.4 \text{ T}) (1.0 \times 10^{-2} \text{ m})^2 (2\pi \cdot 60 \text{ Hz})$$

$$\mathcal{E}_{\text{Max}} = 15 \text{ V}$$