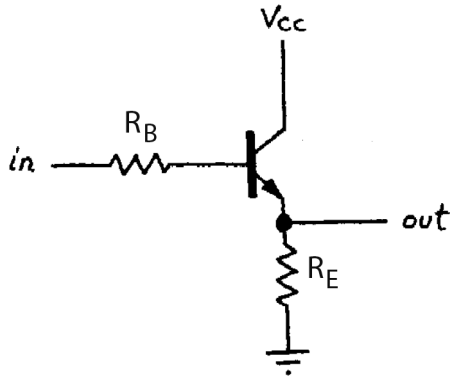


## Physics 120 - David Kleinfeld Spring 2015

### Sketch of the emitter-follower, a unity gain impedance buffer



This circuit can be understood by applying Kirchhoff's voltage law to the left-hand loop. We have:

$$-V_{in} + I_B R_B + V_{BE} + I_E R_E = 0.$$

In the linear regime,  $I_E = (1+\beta)I_B$  so:

$$V_{out} = I_E R_E = (V_{in} - V_{BE}) R_E / [R_E + R_B / (1+\beta)] \approx V_{in} - V_{BE}$$

since  $\beta \gg 1$ . To within an offset of  $V_{BE}$ , the magnitude of output is the same as the input.

The input resistance, found by opening the dependent current source  $I_c$  and shorting the voltage drop  $V_{BE}$ , is just:

$$R_{in} = V_B / I_B = I_E R_E / I_B = (1+\beta) R_E.$$

So we see that the emitter-follower functions as a high impedance input.

The output resistance, found similarly by opening the dependent current source  $I_c$  and shorting the voltage sources  $V_{BE}$  and  $V_{in}$ , is just

$$R_{out} = V_E / I_E = I_B R_B / I_E = R_B / (1+\beta).$$

This is just the resistance of the source divided by the gain.

Both relations generalize to

$$Z_{in} = (1+\beta) Z_E.$$

and

$$Z_{out} = Z_{source} / (1+\beta).$$