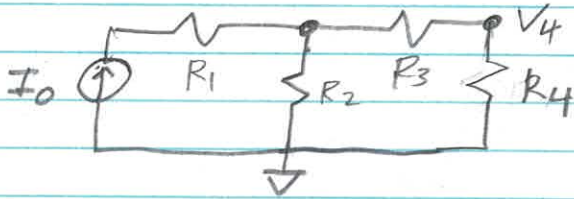


Physics 120 - Spring 2019


- ① Find V_4 in terms of I_0 , R_1 , R_2 , R_3 & R_4



- ② Find V for the Wheatstone bridge circuit



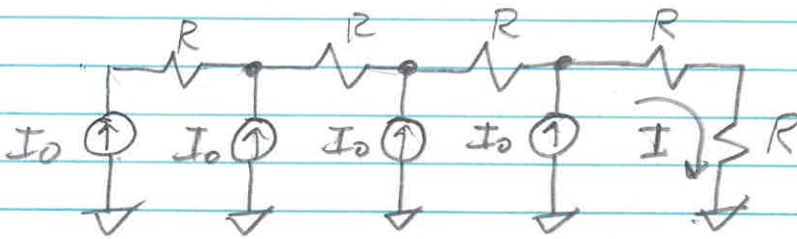- ③ For the wheatstone bridge, let $R_1 = R_2 = R_3 \equiv R$ and $R_4 = R + \delta R$, with $\delta R \ll R$. Find an expression for V to first order in δR . Recall the expression $(1 + \epsilon)^n = 1 + n\epsilon + \dots$.
- ④ Solve for I in terms of I_0 .



- ⑤ Find the Thevenin equivalent circuits between A & A'

