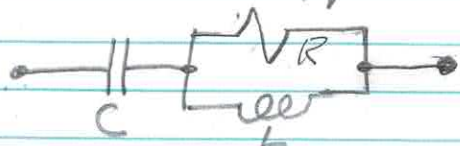


- ① Write an expression for the complex impedance, $\hat{Z}(\omega)$, of




- ② Plot $|\hat{Z}(\omega)|$ vs ω on a log-log plot (Bode plot).
 Identify the break frequencies.
 Identify $|\hat{Z}(\omega)|$ as $\omega \rightarrow 0$.
 Identify $|\hat{Z}(\omega)|$ as $\omega \rightarrow \infty$.

- ③ Write an expression for the complex impedance of:




Plot $\log|\hat{Z}(\omega)|$ vs $\log \omega$ (Bode plot).
 Plot $\text{atan}[\hat{Z}(\omega)] \equiv \text{atan}[\text{Im}(\hat{Z}(\omega))/\text{Re}(\hat{Z}(\omega))]$ vs $\log \omega$;
 this is a plot of the phase shift.

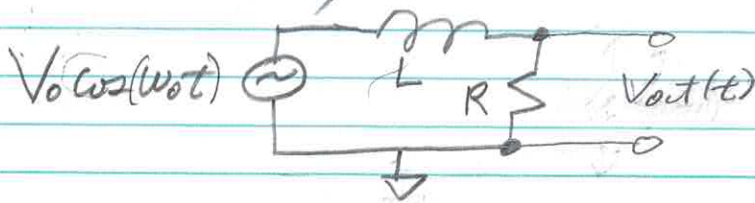- ④ Find the steady state value of $V_{\text{out}}(t)$ in:



Use either the convolution or the Fourier transform method - your choice! Let $\tau \equiv L/R$ for algebraic simplicity.

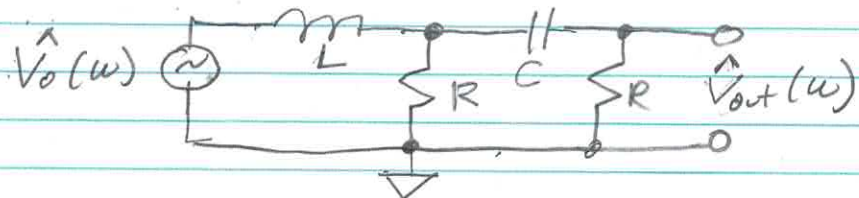- ⑤ Find the steady state value of $\hat{V}_{\text{out}}(\omega)$ in:



Let $a \equiv R/L$ and $b \equiv 1/\tau c$ for algebraic simplicity.

- ⑥ Plot $\log|\hat{V}_{\text{out}}(\omega)|/|\hat{V}_0(\omega)|$ vs $\log \omega$ for the case of $a=b$.