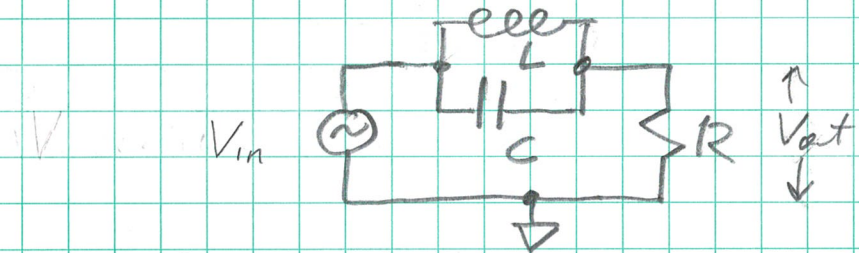



①



Find  $\frac{V_{out}(\omega)}{V_{in}(\omega)}$  and plot the magnitude (log-log) and the phase (linear-log) as a function of frequency.

For  $V_{in}(t) = V_0 \sin \omega t$ , find  $V_{out}(t)$  in steady state.  
Hint: See equations 1.10-1.13 in "Notes on Spectral Domain"

②

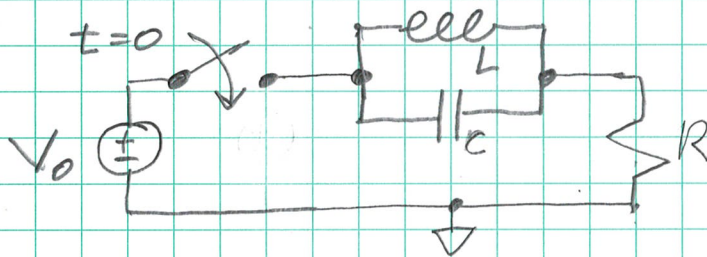

- The switch is closed at  $t=0$
- $V_C(0^-) = 0$

Draw the circuit at  $t=0^+$ , i.e., just after the switch is closed.

Draw the circuit as  $t \rightarrow \infty$ .

Write down the circuit equation, take the Laplace transform, and derive an expression for  $V(s)$ .

Solve for  $V(t)$  by taking the inverse Laplace transform of  $V(s)$ . Hint: see section 1.2 in "Notes on Laplace..."

③ A "switched" power supply makes use of the truncated waveform  $V(t) = \begin{cases} V_0 \sin \omega t & 0 < t \leq T/4 \\ 0 & T/4 < t \leq T \end{cases}$  with  $\omega = 2\pi/T$ .

Continued on Page \_\_\_\_\_

Calculate the coefficients  $\hat{c}_k$  in its Fourier series.  
Hint: See equation 1.8 in "Notes on Fourier Series" and recall  $e^{\pm i\pi k} = (-1)^k$ , etc.