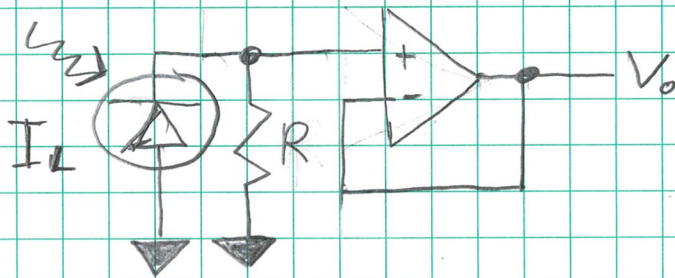


A photodiode is connected to a load resistor, R , and the potential drop is sensed, by a unity gain amplifier



- ① What is V_o for the photocurrent I_L ?
- ② Make a noise model for the circuit, i.e., add a thermal noise for " R " and replace the photodiode with a source of shot noise current. Draw the circuit. Hint: See "Handout on Noise".
- ③ What is the expression for the RMS noise output, denoted δV_o ? Hint: Variances add.
- ④ What is the expression for the signal-to-noise ratio, denoted S/N .
- ⑤ Plot $\log(S/N)$ vs $\log(I_p)$. What happens near $I_p \approx \frac{2k_B T}{e} R$?

In addition, complete problems 1-3 in the handout "Notes on an Op-Amp Differentiator Circuit"

Continued on Page

Read and Understood By

Signed

Date

Signed

Date