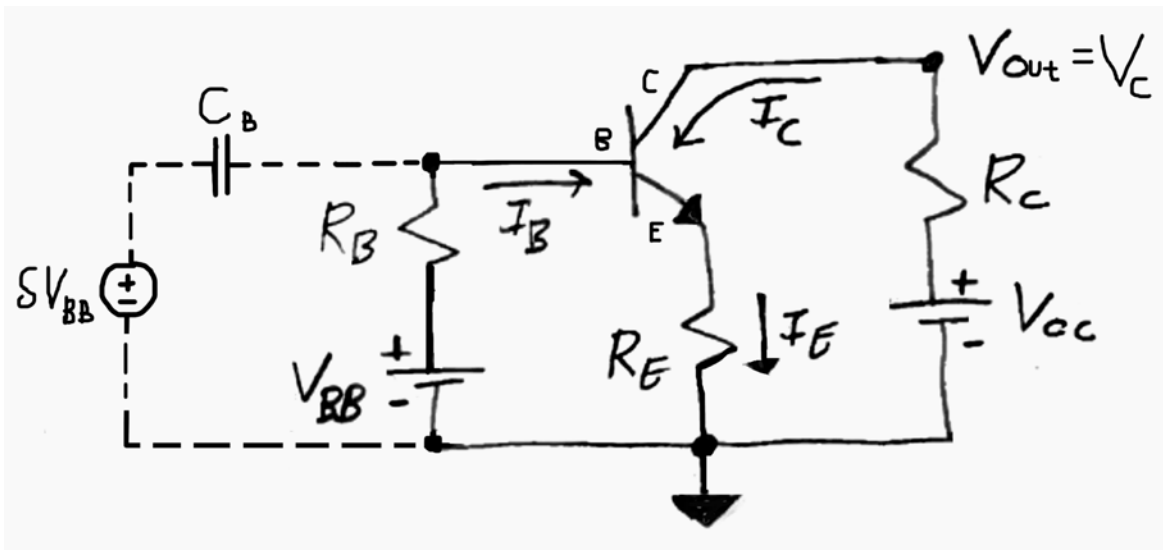


Physics 120 - David Kleinfeld - Spring 2015

Notes on common emitter transistor amplifier (accompanies Laboratory 8).

Here we use the transistor as a voltage amplifier. The idea is to turn a voltage at the input into a current through the base (B), and then turn the current flow through the transistor, *i.e.*, collector (C) to emitter (E) into a voltage drop. Since the dependent current source $I_C = \beta I_B$ can attain any voltage drop, the output is taken at the collector.

Our initial focus is on the DC properties, *i.e.*, setting up the bias to keep the transistor in the roughly "centered" in the active region. As an important technical aside, we use a nonzero value of R_E so that variations in the value of β can be removed to first approximation.



The left hand loop

$$-V_{BB} + I_B R_B + v_{BE} + I_E R_E = 0$$

$$\text{but } I_B = \frac{1}{\beta} I_C \text{ and } I_E = \frac{1+\beta}{\beta} I_C$$

$$\text{so } I_C = \frac{\beta}{1+\beta} \frac{V_{BB} - v_{BE}}{R_E + R_B/(1+\beta)}$$

Recall that $\beta \gg 1$ ($\beta \sim 200$ in this exercise) and choose $R_B \ll (1+\beta)R_E$. Then

$$I_C \simeq \frac{V_{BB} - v_{BE}}{R_E}$$

The right hand loop

$$-V_{CC} + I_C R_C + V_{CE} + I_E R_E = 0$$

$$\text{but } I_E = \frac{1+\beta}{\beta} I_C \simeq I_C$$

$$\text{so } I_C \simeq \frac{V_{CC} - V_{CE}}{R_E + R_C}$$

This equation defines the "load line" for the transistor, *i.e.*, the relation between I_C and V_{CE} that must be satisfied in addition to the intrinsic relation between I_C and V_{CE} that results from the transistor properties.

The output voltage is given by $V_C = V_{CE} + I_E R_E$. Thus

$$\begin{aligned} V_C &\simeq V_{CC} - I_C (R_E + R_C) + I_C R_E \\ &= V_{CC} - I_C R_C \\ &= V_{CC} - \frac{V_{BB} - V_{BE}}{R_E} R_C \\ &= \left(V_{CC} + \frac{R_C}{R_E} V_{BE} \right) - \frac{R_C}{R_E} V_{BB} \end{aligned}$$


The term in the brackets is just a constant. The term proportional to V_{BB} contains a potential signal term. That is, if we change the base voltage source, such as by addition an AC current to the base through the inclusion of a time varying signals δV_{BB} (see previous figure), there is a corresponding change in the voltage at the collector, *i.e.*,

$$\delta V_C \simeq -\frac{R_C}{R_E} \delta V_{BB}$$

The ratio " $-R_C/R_E$ " is the voltage gain. The minus means that the signal is inverted. Notice how β does not play a role (so long as $\beta \gg 1$)! This is the hallmark of good design - factor out the exact value of the gain since this is large but variable from device to device.

Load line and set point

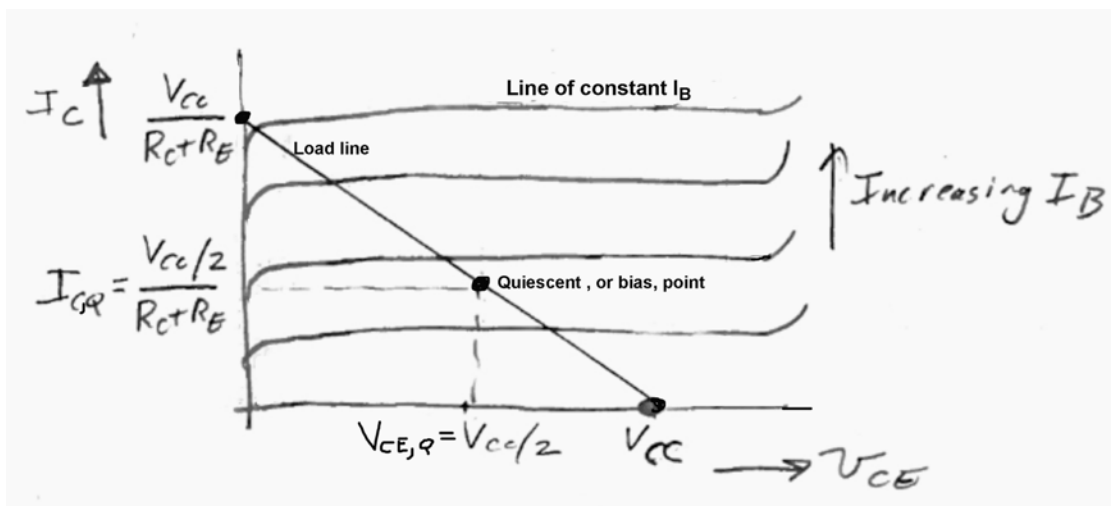The set-point are the values of I_C and V_{CE} , denoted $I_{C,Q}$ and $V_{CE,Q}$, in the absence of AC input. We plot the load line equation (above) on top of the I_C versus V_{CE} curves for this transistor (see attached sheet for a small part of the measured relation) to establish the set-point.



The value of V_{CE} is bounded at the low end by the cut-off voltage of 0.2 V. From the load line equation $I_C \approx \frac{V_{CC} - V_{CE}}{R_E + R_C}$, we see that V_{CE} is bounded from above to be V_{CC} (typically many Volts). Since $V_{CC} \gg 0.2$ V, we choose $V_{CEQ} = V_{CC}/2$ to insure a (near) maximum voltage swing.

Selecting values

Choose the gain. For $|\text{Gain}| = 10$, $R_C = 10 R_E$.

Satisfy $R_B \ll \beta R_E$. Since $\beta \geq 100$, select $R_B = 10 R_E$.

Pick V_{CQ} . We choose $V_{CQ} = 7.5$ V. Then $V_{CC} = 2 V_{CQ} = 15$ V.

Pick I_{CQ} . We choose $I_{CQ} = 1$ mA.

Satisfy the load-line relation $I_{CQ} \approx \frac{V_{CC} - V_{CEQ}}{R_E + R_C} \approx \frac{V_{CC}}{2R_C}$ which yields $R_C \approx \frac{V_{CC}}{2I_{CQ}}$.

Picking standard values of resistors gives:

$$R_C \approx \frac{15\text{V}}{2\text{mA}} \sim 6.8 \text{ k}\Omega,$$

$$R_E \approx \frac{R_C}{10} \sim 680 \Omega,$$

and


$$R_B \approx 10 R_E \sim 6.8 \text{ k}\Omega.$$

Lastly,


$$V_{BB} \approx v_{BE} + I_E R_E \sim 1.5 \text{ V}.$$

Convert from dual to single power supply

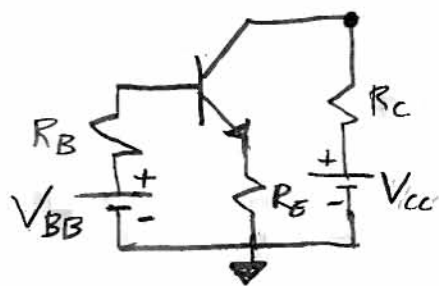
Rather than have two batteries, we use one battery for both V_{BB} and V_{CC} . Since V_{CC} is the larger voltage, we use it as the supply. and build a voltage divider to replace V_{BB} and R_B .



Original

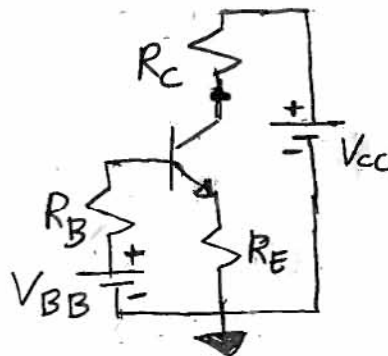

Still Original

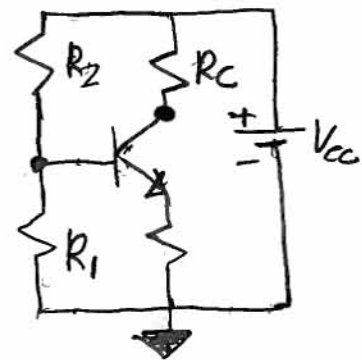

Transformed

From the diagrams above,

$$R_B \simeq \frac{R_1 R_2}{R_1 + R_2} \quad \text{and} \quad V_{BB} \simeq \frac{R_1}{R_1 + R_2} V_{CC}$$

so that

$$R_1 \simeq R_B \frac{V_{CC}}{V_{CC} - V_{BB}} \quad \text{and} \quad R_2 \simeq R_B \frac{V_{CC}}{V_{BB}}$$

Substituting in values and using standard components gives:

$$R_1 \simeq 5.6 \text{ k}\Omega \frac{15\text{V}}{15\text{V} - 1.5\text{V}} \sim 5.6 \text{ k}\Omega \quad \text{and} \quad R_2 \simeq 5.6 \text{ k}\Omega \frac{15\text{V}}{1.5\text{V}} \sim 56 \text{ k}\Omega$$

Lastly, must also satisfy $R_1 \ll R_{in}$, *i.e.*, $R_1 \ll \beta R_E$, so that the input resistance does not contribute to the voltage divider. Our choices lead to self-consistency with $5.6 \text{ k}\Omega \ll 200 \times 680 \Omega$ or $5.6 \text{ k}\Omega \ll 140 \text{ k}\Omega$, so all is fine.

Coupling of the AC signal, δV_{BB} .

This signal is high pass filtered with a cut-on frequency of $1/(2\pi R_B C_B)$. The desired cut-on frequency, f_C , sets the value of C_B , by $C_B = 1/(2\pi f_C R_B)$.

Fini!