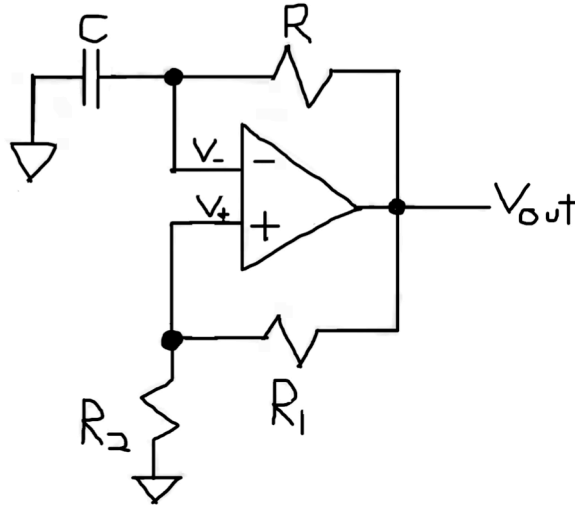


## Notes on Relaxation Oscillators

Physics 120, David Kleinfeld, Spring 2018

This is a basic oscillator circuit in which the voltage across a capacitor relaxes toward a time varying target voltage. Consider the circuit below, using a high gain op-amp as a comparator:



The time-varying voltage at  $V_+$  serves as a target level that is a fraction  $R_2/(R_1+R_2)$  of the output voltage  $V_{out}$ . The time-varying voltage at  $V_-$  heads toward this value and when it exceeds the value, the output of the amplifier changes sign, thus the target changes sign, and the voltage at  $V_-$  heads toward this new value.

We know that  $V_{out} = A(V_+ - V_-)$  where  $A \gg 1$ .

Since  $V_{out}$  is bounded by  $V_{supply}$ , this means that

$$V_{out} = \begin{cases} +V_{supply} & V_+ > V_- \\ -V_{supply} & V_- < V_+ \end{cases}$$

The voltage divider assures that the value of  $V_-$ , which can asymptote at  $V_- = V_{out}$ , will be compared to a value for  $V_+$  that is smaller than  $V_{out}$ , i.e.,  $V_+ = \frac{R_2}{R_1+R_2} V_{out}$ .

$V_-(t)$  will evolve in time according to:

$$C \frac{dV_-}{dt} + \frac{V_- - V_{out}}{R} = 0$$

with  $\tau \equiv RC$ . Thus:

$$\frac{dV_-}{dt} + \frac{1}{\tau} V_- = \frac{1}{\tau} V_{out}$$

The solution to this homogeneous part of this equation is:

$$V_-(t) = V_-(0)e^{-t/\tau}.$$

so that the full solution is:


$$V_-(t) = V_-(0)e^{-t/\tau} + \int_0^t \left(\frac{1}{\tau} V_{out}\right) e^{-(t-x)/\tau} dx.$$

We take  $t = 0$  as the time of the last transition and consider the interval of time up to the next transition, i.e.,  $t = T/2$ , so that  $V_{out}$  is a constant. The value of  $V_-(0)$  just after the transition, i.e.,  $V_-(0^+)$ , is opposite in sign to that of  $V_{out}$ , so

$$V_-(0) = -\frac{R_2}{R_1 + R_2} V_{out}.$$

Thus:
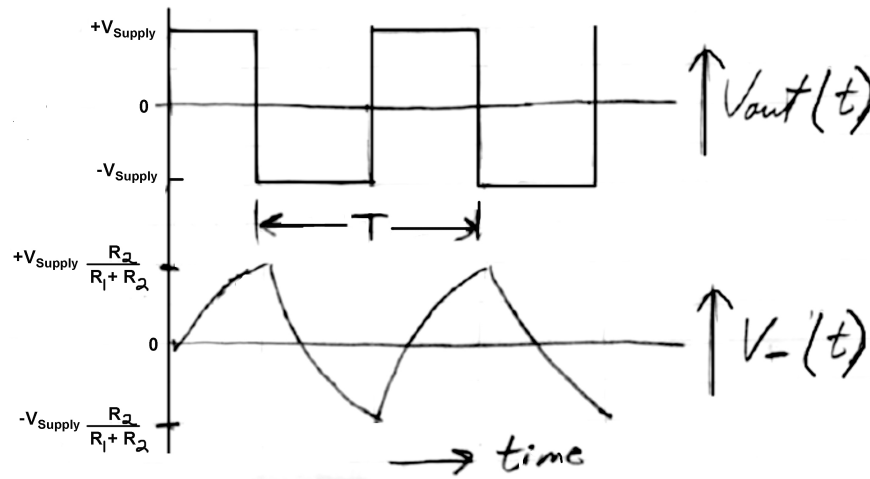
$$V_-(t) = -\frac{R_2}{R_1 + R_2} V_{out} e^{-t/\tau} + V_{out}(1 - e^{-t/\tau})$$



At  $t = T/2$  the value of  $V_-(t)$  will reach the threshold level

$$V_-\left(\frac{T}{2}\right) = +\frac{R_2}{R_1 + R_2} V_{out}$$

so

$$\frac{R_2}{R_1 + R_2} V_{out} = -\frac{R_2}{R_1 + R_2} V_{out} e^{-T/2\tau} + V_{out} \left(1 - e^{-T/2\tau}\right)$$

or

$$T = 2\tau \log\left(1 + 2\frac{R_2}{R_1}\right).$$

As a partial check, when  $R_2 \rightarrow \infty$  we have  $T \rightarrow \infty$ .

Also, when  $R_2 \rightarrow 0$  we have  $T \rightarrow 4\tau \left(\frac{R_2}{R_1}\right)$ .