

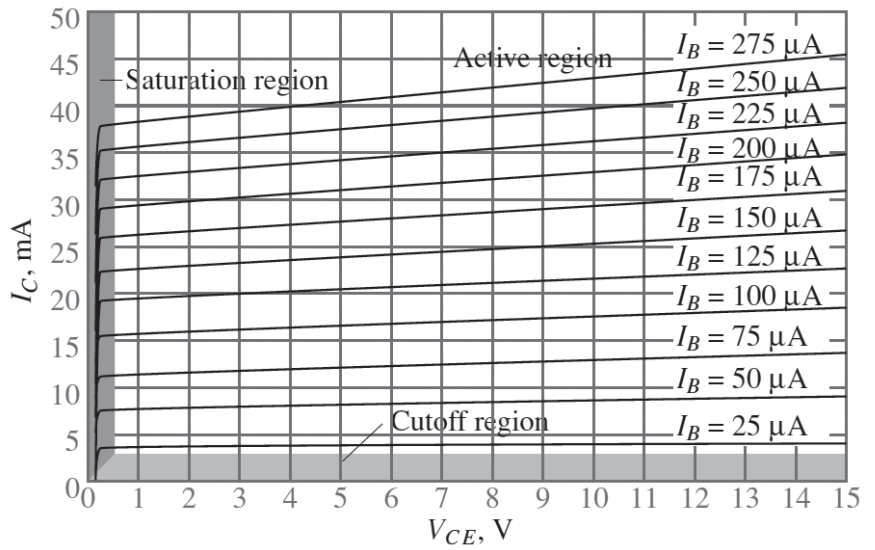
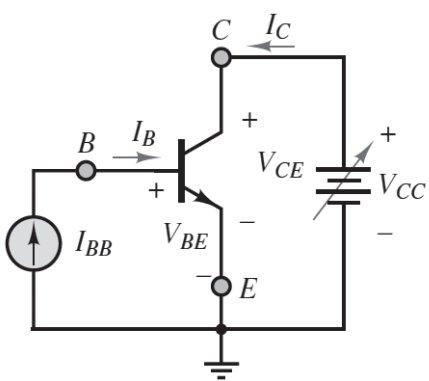
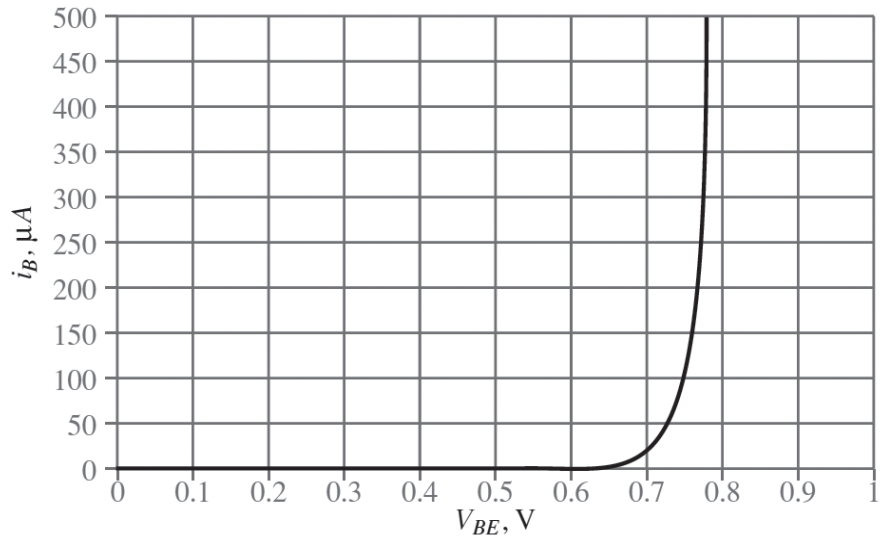


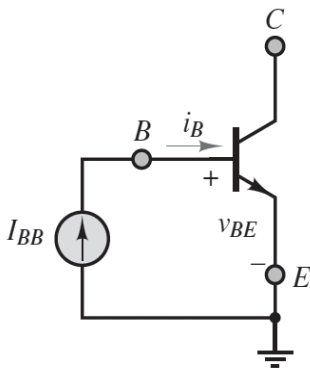KCL: $i_E = i_B + i_C$
 KVL: $v_{CE} = v_{CB} + v_{BE}$



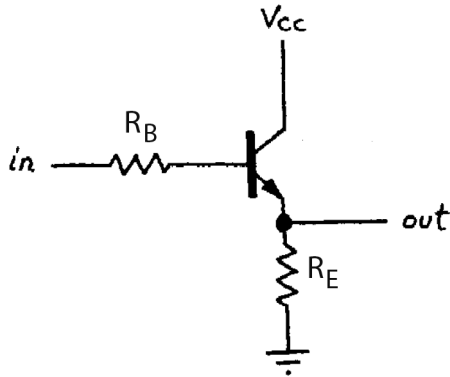Sketch of the emitter-follower, a unity gain impedance buffer.



This circuit can be understood by applying Kirchhoff's voltage law to the left-hand loop. We have:

$$-V_{in} + I_B R_B + V_{BE} + I_E R_E = 0.$$

In the linear regime, $I_E = (1+\beta)I_B$ so:

$$V_{out} = I_E R_E = (V_{in} - V_{BE}) R_E / [R_E + R_B / (1+\beta)] \approx V_{in} - V_{BE}$$

since $\beta \gg 1$. To within an offset of V_{BE} , the magnitude of output is the same as the input.

The input impedance, found by opening the current source I_C and shorting the voltage drop V_{BE} is just:

$$Z_{in} = V_B / I_B = I_E R_E / [I_E / (1+\beta)] = (1+\beta) R_E.$$

So we see that the emitter-follower functions as a high impedance input.

The output impedance is approximated by $Z_{out} \approx V_{source} / \beta$.
Can you show this?