Week 5 Homework

Physics 1B

February 6, 2007

1 Serway C17.5

The car battery has some internal resistance (which doesn't change, since it's a property of the battery). The starter draws a large current from the battery, which causes a very large voltage drop across the internal resistance of the battery. This leaves less voltage for things like the headlights, since the voltage drop across an entire closed loop must still be zero. This reduced voltage across the headlights causes them to dim.

2 Serway C17.7

Batteries can be placed in many different circuits (remote controls, Furbies, Aquatine Hunger Force ads, etc.) which all may have different resistances. Because we don't know the resistance in the circuit the battery will be used, we don't know the current it will produce. Appliances, on the other hand, have a given resistance, so we can calculate the current.

3 Serway C17.9

Although connecting batteries in parallel doesn't increase the voltage, it does increase the ability to output current (and therefore, since P=IV, power).

4 Serway C17.19

So long as the parachutist does not bridge a gap between a high and low voltage, she will not be electrocuted. Therefore, when she holds only the power line, she is safe. However, if she holds the power line while touching the ground, she completes the circuit, and will be hurt.

5 Serway C17.21

b) When the switch is closed, current has an easy way to make it back to the battery (by bypassing lamp C), so that's the way the current goes. Correspond-

ingly, lamp C goes out (zero intensity).

d) Since there is no current through lamp C, the voltage drop across lamp C is also 0. Therefore, the voltage drops across A and B must increase so that the net voltage drop for the circuit is still 0.

a) Because the voltages across A and B increase, the power dissipated by each of them increases. Therefore, their intensities increase as well.

c) Because the total resistance of the circuit goes down, but the voltage drop across the circuit is the same, the current in the circuit goes up.

e) We can tell that the power increases because $P = IV = V^2/R$. The voltage drop across the circuit doesn't change when closing the switch, but the net resistance decreases. Therefore the total power dissipated increases.

Chapter 18



Odince this branch doesn't lead anywhere, no current passes through it. Therefore it doesn't add to the equivalent

Υ.

resistance.

AG in parallel:

Reguts R4 R5

Req = R

These resistors are all in series, so

$$R_{eq} = R + R + R_{eq} + s$$
$$= R + R + \frac{R}{2}$$

$$Reg = \frac{5}{2}R$$





· Resistors () and () are in series, so Royts = RytRs. We can redraw the picture

OR





OS
Now we can easily see that (2,3), and (36) are
in parallel, so Regards:

$$\frac{1}{R_{eqysts}} = \frac{1}{R_{x}} + \frac{1}{R_{3}} + \frac{1}{R_{4s}}$$

$$= \frac{1}{10R} + \frac{1}{SR} + \frac{1}{2SR}$$

$$R_{eqysts} = \frac{50}{17R} = 2.94 \text{ A}$$

$$M_{HH} = R_{eq} = R_{1} + R_{eqysts}$$

$$= 10R + \frac{50}{17R}$$



WeekSHW

(9.)
$$\Delta V_{acrossO} = (1.93 \text{ A})(10 \Omega) = V_{O}$$

= 19.3 V
 $\Delta V_{acrossOS}$: $V_{OS} = V_{O} = V_{O} = V_{S} = V - V_{O}$ in parallel, voltage
drop same across
all branches.
 $\Delta V_{OS} = V - V_{O} = 25.0V - 19.3V = 5.7V$

· Current through (DE) = 14:



84

$$\frac{1_{3}}{1_{4}} = \frac{1_{2}}{1_{4}} = \frac{V_{0}}{R_{0}} = \frac{5.7V}{10.0\Omega} = 0.57 \text{ A}$$

$$\frac{1_{3}}{1_{3}} = \frac{V_{0}}{R_{0}} = \frac{5.7V}{5.00\Omega} = 1.14 \text{ A}$$

$$\frac{1_{4}}{1_{4}} = \frac{V_{00}}{R_{0}} = \frac{5.7V}{25.0\Omega} = 0.23 \text{ A}$$

$$\frac{1_{4}}{R_{eq+5}} = \frac{5.7V}{25.0\Omega} = 0.23 \text{ A}$$
Current through branch 4 is current through 20.0 \Omega resin tor.
Check $1 = 1_{2} + 1_{3} + 1_{4}$ (junction rule)
$$1.93 \text{ A} = 0.57 \text{ A} + 1.14 \text{ A} + 0.23 \text{ A}$$

- -

5 HW Week



/-.



resistors: $P_{4\Omega} = (2.67A)^2 (4\Omega) = 28.4W$ $P_{4\Omega} = (2.67A)^2 (2\Omega) = 14.2W$

•

Week 5 HW

¥2

.

(44.)
$$\Delta V_{loop} = 0$$

 $\Delta V_{resistor} = 1R$
 $\sim Looking at the inner loop $_{18V} = 1000$
 $+\Omega$
 $\Delta V_{loop} = +18V + \Delta V_{2\Omega} + \Delta V_{3\Omega} + \Delta V_{4\Omega}$
 $= 0$$

AV_{3.2} = 1.0 vite = 2V Because the 3.0 and 1.0 resistor are in parallel, $\Delta V_{1.0} = 2.V$ (same as $\Delta V_{3.0}$). P_{1.0} = $\frac{V^2}{R}$ $= \frac{(2.V)^2}{3.0}$ $P_{3.0} = 1.33.VV$ $P_{1.0} = 4.00.VV$

-

Week 5 HW





ousing this trick, we can make a 25 sl resistor from two SOSL resistors. Putting that in series with a 2012 resistor gives the desired resistance:

son
$$\frac{1}{1}$$
 son $\frac{1}{1}$ Req = 45 Ω

b) ohike in (a), we can make a 100 resistor by putting two 20sh resistors in parallel. Putting this in series

with our
$$25 \Omega$$
 resistor from part (a)
yields $R_{eq} = 35 \Omega$
 $20\Lambda \frac{5}{2} \frac{2}{2}20\Lambda$
 $50\Lambda \frac{5}{2} \frac{2}{5}50\Lambda$
 35Ω





picture are
$$\Delta V_{SR} = (0.2R)(2\Omega) = 0.4V$$

 $\Delta V_{2R} = (0.2R)(2\Omega) = 0.4V$
 $\Delta V_{10R} = (0.2R)(10\Omega) = 2V$

.

Week 5 HW



circuit :

- * The choice to fix one voltage value is arbitrary. we choose V=0 Here
 - at t.

across the middle branch is . The voltage

$$V_{ab} = 5.4 V$$

1000

.





· Looking at outer loop of right circuit,

$$AN_{100p} = 0$$

 $= 24 V - (1, 1)(6 \Omega) - (1_3)(6 \Omega) + 12V$

$$1_1 + 1_3 = 6 R$$
 (.)

8

• Looking at top loop of right circuit,

$$\Delta N_{100p} = 0$$

$$= 24V - (1,)(6\Omega) - (1_2)(3\Omega)$$

$$I_1 + \frac{1}{2}I_2 = 4R$$

$$2I_1 + I_2 = 8R$$
(2)
• Applying Kirchoff's junction rule,

$$I_1 = I_2 + I_3$$
(3)

• Substituting (3) into (1) and (2)

$$(12+1_3)+1_3 = 6A$$

 $1_2+21_3 = 6A$ (1)
 $2(1_2+1_3)+1_2 = 8A$
 $31_2+21_3 = 8A$ (2)
• Subtracting (1) from (2),
 $21_2 = 2A$
 $1_2 = 10A$

.

(25).
$$\circ$$
 Substituting into (27)
 $3(1 A) + 2I_3 = SA$
 $\boxed{I_3 = 2.5 A}$
 \circ Substituting into (3),
 $I_1 = (1.0 A) + (2.5 A)$
 $\boxed{I_1 = 3.5 A}$

Ϋ́



6. T

o How much charge a capacitor has on its plates is proportional to the voltage across it at any given time. We know that the charge on the capacitor at time t is given 57

8

$$q = Q(1 - e^{-t/RC})$$

where Q is the capacitor's charge once it is
fully charged. When it is fully charged,
current no longer flows, and the voltage
across the capacitor is the same as the
battery's voltage. is
$$Q = C(12N)$$
.
battery's voltage across capacitor at
time t. is $Q = CV$. Substituting,

$$CV = C(12v)(1 - e^{-t/RC})$$

$$\frac{\sqrt{1}}{12\sqrt{1}} = 1 - e^{-t/RC}$$

$$R = 12 \times 10^3 \Omega$$

At t= 15, $V = 10 V$.

1

$$S_{ubstituting}, -(1 s)/(12 \times 10^{2} \Omega) c$$

$$\frac{10 V}{12V} = 1 - e$$

$$1 - \frac{5}{6} = e^{-(1 s)/(12 \times 10^{2} \Omega) c}$$

$$1 - \frac{5}{6} = e^{-(1 s)/(12 \times 10^{2} \Omega) c}$$

$$1 - (1 s) = \frac{-(1 s)}{(12 \times 10^{3} \Omega) c} \longrightarrow [c = 4.7 \times 10^{-5} F]$$

Week 5 HW

a) 36.° Oince the enf of the battery is thou, the maximum voltage across the capacitor will be the Unit it is fully charged).

$$V = \frac{1}{2}R$$

 $R = \frac{1}{1} = \frac{48.0V}{0.500\times10^{-3}A} = 96 K\Omega$
A at start of
problem, capacitor
 $acts like a$
wire.

*

$$2 = RC = 7 C = 7R = \frac{0.9600}{9.6 \times 10^{4} \Omega}$$

$$C = 1.0 \times 10^{-5} F$$

b)
$$q = Q(1 - e^{-\frac{\pi}{Rc}})$$

= $(1.0 \times 10^{-5} F)(48.0 V)(1 - e^{-1.925/0.9605})$



Week S HW



 $Ceq = C_1 + C_2$ $\frac{1}{Req} = \frac{1}{R_1} + \frac{1}{R_2}$ Ceq = 5.0 MF Reg = 1.2 KS2

Looking at right circuit, as in #34,36, -t/Rc)

$$V = Q (1 - e^{-t/pc})$$

= Ceq E (1 - e^{-t/pc})
= (5.0 \mu F)(120V)(1 - e^{-t/(1.2 \times 10^3 R)(5.0 \times 10^{-6} F)})
= (6 \times 10^{-4} C)(1 - e^{-t/(6 \times 10^{-3} S)})

$$Q = CV \implies V = \frac{9}{c_{eq}} = \frac{(6 \times 10^{-4} \text{ c})}{(5.0 \text{ MF})} (1 - e^{-\frac{1}{6}(\times 10^{-5} \text{ s})}$$
This is the voltage across the
capacitors at any time t.
$$V = (20 \text{ V}) (1 - e^{-\frac{1}{6}(\times 10^{-5} \text{ s})})$$
Using $q = CV$ for each capacitor,
$$Q_1 = (2.0 \times 10^{-6} \text{ F})(120 \text{ V})(1 - e^{-\frac{1}{6}(\times 10^{-5} \text{ s})})$$

$$Q_2 = (3.0 \times 10^{-6} \text{ F})(120 \text{ V})(1 - e^{-\frac{1}{6}(\times 10^{-5} \text{ s})})$$

Restatement of 18.41

A mylinated axon can be modeled as a cylindrical capacitor with the parallel plate

following parameters:

$$d = 10 \text{ cm} \\ d = 1.0 \times 10^{-8} \text{ m} \\ K = 3.0 \\ r = 10 \text{ } \text{m}$$

Recall that for a parallel plate capacitor, $C = \frac{1}{4\pi K_e} \cdot \frac{A}{d}$. Here the area of a plate is the surface area of the cylinder.

a) From fig. 18.28, when the ion is not conducting an electric pulse, the potential difference across it is 70mV. How many Kt ions are outside the axon? Is this a large charge per unit area? (see hint in book).

See book for parts (b) through (d)

Week 5 HW

41. a)
$$Q = CV$$

$$C = \frac{K}{4\pi K_{e}} = \frac{A}{d}$$
where $A = 2\pi T r_{e}^{4} = 0.3 \times 10^{-6} m^{2}$

$$Q = \frac{AVK}{4\pi K_{e} d}$$

$$= \frac{2\pi T (10 \times 10^{-6} m)(10 \times 10^{-2} m)(10 \times 10^{-2} v)(5.0)}{4\pi T (5.99 \times 10^{-9} N m_{e}^{2})(1.0 \times 10^{-9} m)}$$

$$Q = 1.2 \times 10^{-9} C$$

$$= Poreassium ion has a net charge of te, and this is $\frac{1.2 \times 10^{-9} m}{1.6 \times 10^{-10}} = 7.3 \times 10^{-9} ions.$

$$= 0.3 \times 10^{-6} m^{2} = 6.3 \times 10^{14} A^{2}$$

$$= 1.2 \times 10^{-5} ions / square angeuron$$

$$= 1.7 \times 10^{-9} C$$

$$= 1.8 \times 10^{-7} A$$$$

d) PE = q VV = (b) - (-70) mV = 100 mV

١