

Physics 1B - Quiz 3 (12 Feb 2007)

Formulas

The force on charge q_1 from charge q_2 is $\vec{F}_{12} = k_e \frac{q_1 q_2}{r_{12}^2} \hat{r}_{12}$, where the direction vector \hat{r}_{12} points from q_2 to q_1 and the proportionality constant is $k_e = 8.99 \times 10^9 \text{ Nm}^2/\text{C}^2$.

Note that the permittivity of free space is $\epsilon_0 \equiv \frac{1}{4\pi k_e} = 8.85 \times 10^{-12} \text{ C}^2/(\text{Nm}^2) = 8.85 \times 10^{-12} \text{ A}^2 \text{s}^4/(\text{kg m}^3)$.

Note that the unit of elemental electronic charge is $e^- = -1.62 \times 10^{-19} \text{ C}$.

The force on a test charge q_0 induced by an electric field, denoted \vec{E} , is $\vec{F} = q_0 \vec{E}$.

The electric flux through a surface is $\Phi_e \equiv \sum_{\text{All Surfaces}} EA_{\perp} = \sum_{\text{All Surfaces}} EA \cos \theta$, where $A_{\perp} = A \cos \theta$ is the component of the area whose normal lies parallel to the electric field..

Gauss' Law relates the net flux through a closed surface to the net charge enclosed by the surface, *i.e.*, $\Phi_e = 4\pi k_e Q_{\text{Total}}$.

The electric field produced by a point charge q at the origin, *i.e.*, $\vec{r} = 0$, is $\vec{E} = k_e \frac{q}{r^2} \hat{r}$ where \hat{r} is the radius vector in spherical coordinates.

The electric field produced by a line charge, with charge per unit length λ , is $\vec{E} = 2k_e \frac{\lambda}{r} \hat{r}$, where the line is defined to lie along the \hat{z} axis and \hat{r} is the radius vector in cylindrical coordinates.

The electric field produced by a surface charge, with charge per unit area σ , is $\vec{E} = 2\pi k_e \sigma \hat{n}$, where the surface lies in the \hat{x} - \hat{y} plane and \hat{z} corresponds to the normal to the \hat{x} - \hat{y} plane in Cartesian coordinates.

Work-Energy Theorem: $W = \Delta KE + \Delta PE$

Electric potential: $\Delta V = -E \Delta x \cos \theta$, where $\Delta V = \frac{\Delta PE}{Q}$

$V = k_e \frac{q}{r}$ a distance r away from a point charge q .

Current: $I = \frac{\Delta Q}{\Delta t}$ or $I = n e v_D A$

Capacitance: $Q = C \Delta V$ where $C = \frac{\kappa}{4\pi k_e} \frac{A}{d}$ for parallel plates and κ is the dielectric constant

$$I = C \frac{\Delta V}{\Delta t}$$

$$\text{Energy Stored} = \frac{1}{2} Q \Delta V = \frac{1}{2} C (\Delta V)^2 = \frac{1}{2C} Q^2$$

Resistance: $V = I R$ where $R = \rho \frac{L}{A}$ and ρ is the resistivity in Ohm-m.

	Series	Parallel
Capacitors	$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$	$C_{eq} = C_1 + C_2 + C_3 + \dots$
Resistors	$R_{eq} = R_1 + R_2 + R_3 + \dots$	$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$

$$\text{Power Dissipated} = IV = I^2 R = V^2/R$$

- Kirchoff's Laws:
- 1) Sum of voltage drops around any loop is zero, *i.e.*, gains = losses
 - 2) Sum of current flow into a node is zero, *i.e.*, total current in = total current out

Finally! The Quiz

1. For current flow in a resistor, which statement is true?
 - A. The acceleration of the charge carrier is proportional to the voltage drop across the resistor
 - B. The velocity of the charge carriers is proportional to the voltage drop
 - C. The velocity of the charge carriers is a constant that depends solely on the type of material
 - D. The velocity of the charge carriers is a constant that depends solely on the temperature
 - E. The velocity of the charge carriers is a constant that depends solely on the geometry
2. A 1.50 V battery is connected across a 4 F capacitor, as shown below in figure 1. What is the energy stored in the capacitor subsequent to removal of the battery?
 - A. 6.0 J
 - B. 4.5 J
 - C. zero
 - D. 6.0 W
 - E. 4.5 W

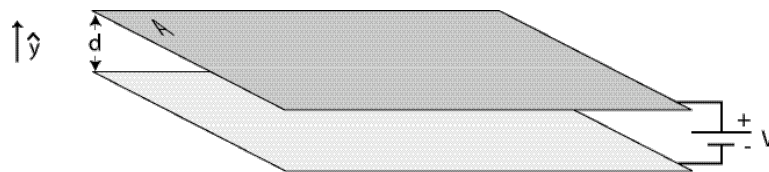


Figure 1

3. The resistivity of cytoplasm, the solution inside of a cell, is $100 \, \Omega \cdot \text{cm}$. What is the resistance of a cylinder of cytoplasm that is 1.0 mm long and $2.0 \, \mu\text{m}$ in diameter? Mind the units!
 - A. $3.2 \times 10^8 \, \Omega$
 - B. $3.1 \times 10^{-15} \, \Omega$
 - C. $3.2 \times 10^3 \, \Omega$
 - D. $8.0 \times 10^7 \, \Omega$
 - E. $8.0 \times 10^3 \, \Omega$

4. A room heater operates at 220 Volts and consumes 2000 W of power. How much current does the heater draw?


- A. 1.1×10^{-1} A
- B. 4.1×10^{-3} A
- C. 3.0 A
- D. 9.1 A
- E. 4.4×10^5 A

5. In bacterial photosynthesis, the absorption of one photon causes a *pair* of electrons to move across the membrane. Under high light levels, *pairs* of *electrons* cross once every $100 \mu\text{s}$. What is the current?

- A. 1.6×10^{-21} A
- B. 3.2×10^{-21} A
- C. 2.0 A
- D. 1.6×10^{-15} A
- E. 3.2×10^{-15} A


6. A battery supplies current to a circuit with 3 resistors, as shown below in figure 2. What is the correct expression for the total current I?

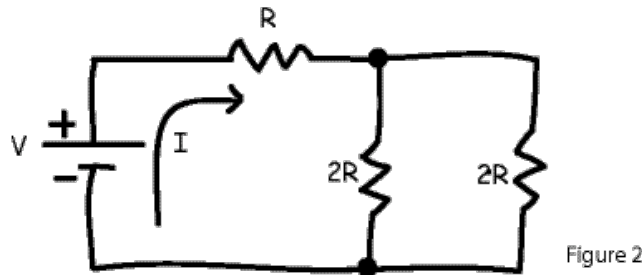- A. V/R
- B. $V/(2R)$
- C. $2V/R$
- D. $5V/4R$
- E. $3V/R$



7. Find the equivalent resistance between points A and B for the circuit shown below in figure 3.

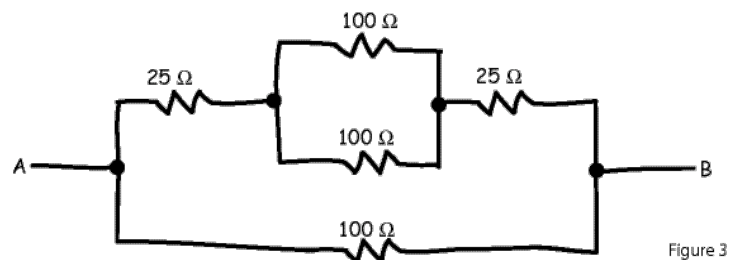- A. 50Ω
- B. $3.0 \times 10^{-2} \Omega$
- C. 112Ω
- D. 71Ω
- E. 3.8Ω



8. A battery supplies current to a circuit with 4 resistors, as shown below in figure 4. What is the correct expression for the potential V_1 ? Hint – you do not need to keep track of V_2 to find V_1 .

- A. $1/3 V_B$
- B. $1/2 V_B$
- C. $2/3 V_B$
- D. $4/5 V_B$
- E. $2 V_B$

9. What is the correct expression for the potential V_2 in Figure 4? Think carefully before you start!

- A. $1/5 V_B$
- B. $1/4 V_B$
- C. $1/3 V_B$
- D. $1/2 V_B$
- E. $2/5 V_B$

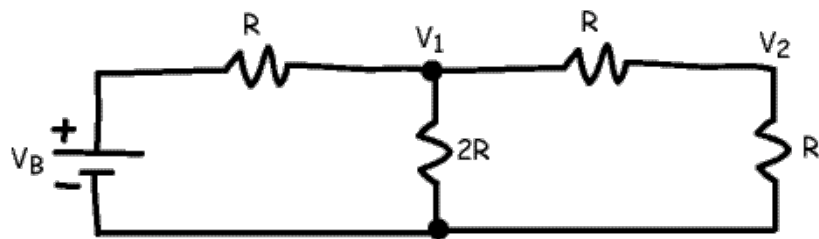


Figure 4

10. In a real battery with interval resistance, as shown below in figure 5, the voltage drop across an external load resistor is

- A. always less than the open circuit voltage, V_{battery}
- B. equal to the open circuit voltage
- C. unconstrained
- D. zero
- E. always greater than the open circuit voltage

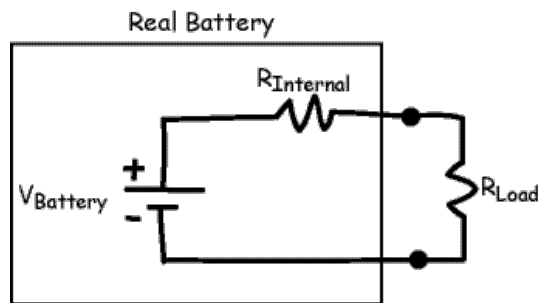


Figure 5