

Homework 3, (Week 4)

In class we found that the natural decay frequency of an underdamped oscillator is $\omega = \sqrt{\omega_0^2 - (1/2\tau)^2}$.

Does this correspond to the resonant frequency of the same system? Let's solve the driven LRC circuit for $v(t)$ in steady state.

$$\frac{d^2 v}{dt^2} + \frac{1}{\tau} \frac{dv}{dt} + \omega_0^2 v = X_0 \sin \omega t$$

Hints: (1) Use $v(t) = V_0 \sin(\omega t + \phi)$ as a trial function.

(2) Recall the expansions for $\cos(a+b)$ and $\sin(a+b)$.

(3) Group terms proportional to $\sin \omega t$ and $\cos \omega t$.

(4) The final result should be in the form

$$v(t) = \frac{X_0}{\text{function}(\omega, \omega_0, \tau)} \sin[\omega t + \phi]$$

Minimize the function of ω , ω_0 , and τ to find the resonant frequency.

Plot the amplitude and phase of $v(t)$ versus frequency as a Bode plot.

State a formula for $\omega_{\text{resonance}} = \text{function}(\omega_0, \tau)$