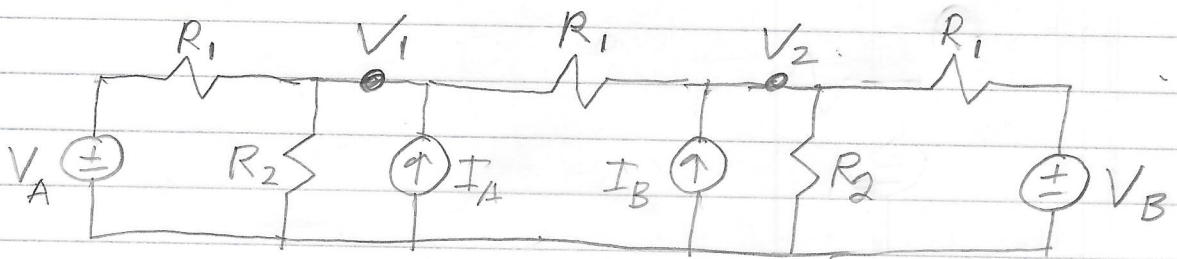



H. W. 1

(1) Solve for  $V_1$  and  $V_2$



Find expressions for  $V_1$  and  $V_2$ .

(2)

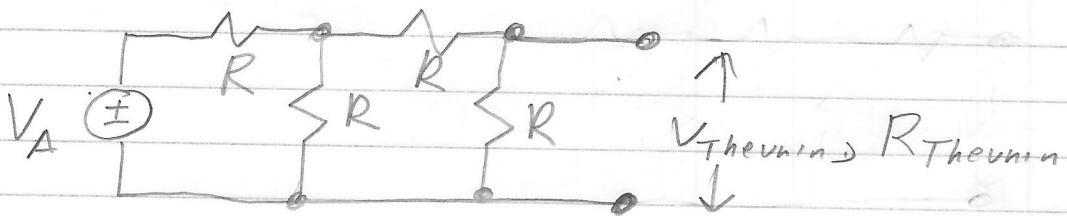

Find the Thevenin equivalent circuit

(3) Why should you check the voltage of a battery using a load?