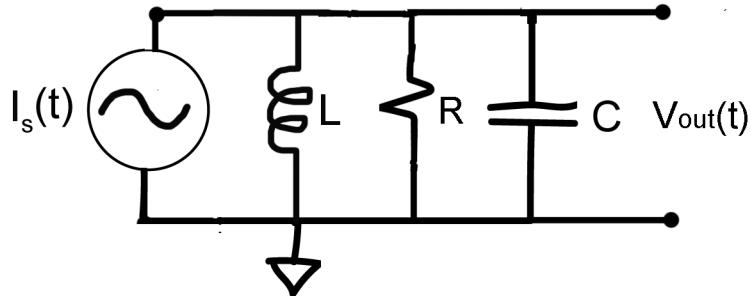


## Homework 5 - Physics 39 L (2026)

The parallel RCL circuit below is excited by an input  $I_s(t)$ .



- (1) Write a differential equation for  $V_{out}(t)$ . Identify scales  $\omega_0$ ,  $\tau_L$ ,  $\tau_R$ .
- (2) Write an algebraic equation for  $V_{out}(\omega)$ .
- (3) What is the asymptotic frequency dependence, in terms of magnitude and phase, of  $V_{out}(\omega)/I_s(\omega)$  as  $\omega \rightarrow 0$ ? As  $\omega \rightarrow \infty$ ?
- (4) Solve for the steady-state value of  $V_{out}(t)$  for a sinusoidal input, i.e.,  $I_s(t) = I_0 \sin \omega t$ .