

# Physics 4L Lab 7 (2026)

## 7.1 Subharmonic generation

Our experimental system is a series L-C-R circuit with a series diode. This leads to interesting behavior indeed. The circuit is driven by a sinusoidal oscillator. It is described by


$$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + V_D = V_0 \sin(2 \pi f t),$$

where  $V_D$  is the voltage across the diode with  $V_D = (k_B T/e) \log[d(Q/I_0)/dt + 1]$  where  $I_0$  is the reverse bias current. Under reverse bias voltage the p-n junction in the diode is swept free of charge and functions as a capacitor to pass an alternating current, with  $C(V) \sim C_J(0)/\sqrt{1-V_D/V_I}$  where  $C_J(0)$  is the junctional bias at zero voltage and  $V_I$  is the junction potential. Under forward bias the diode will conduct and functions as a resistor.

For our realization, we use a 1N4004 diode, with  $C(0) \sim 20 \text{ pF}$  and  $V_I = 0.6 \text{ V}$ . Each coil has a nominal inductance of  $10 \text{ mH}$  and a nominal resistance of  $150 \Omega$ , yielding  $L = 20 \text{ mH}$  and  $R = 300 \Omega$ . At low values of applied voltage, i.e.,  $V_0 \ll k_B T/e = 25 \text{ mV}$ , the system behaves like a resonant circuit. As  $V_0$  is increased,  $C(V)$  decreases and the resonant frequency shifts upward.

It is not our intention to study the intractable non-linear differential equations for this system. Rather we will make measurements to study bifurcations to period doubling, tripling, etc.

Build the circuit (Figure 7.1) and record  $V_{\text{in}}$  and  $V_{\text{out}}$ .

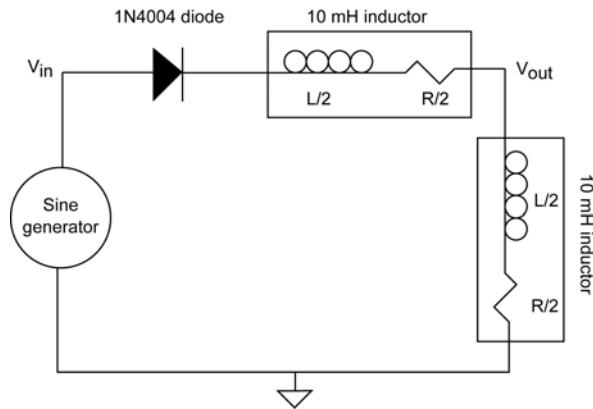

**Figure 7.1.** A circuit to generate subharmonics. Check that the sine generator is on "high impedance" output.

To shake out the basic circuit dynamics, use the "Acquire" function on the oscilloscope to shift the display of the oscilloscope between "X-Y", i.e.,  $V_{\text{out}}$  versus  $V_{\text{in}}$ , and "X-T", i.e., the usual  $V_{\text{in}}$  versus time and  $V_{\text{out}}$  versus time. Set the frequency to about  $1.15 f_0$  and slowly ramp up the voltage.

*Note 1: Transitions occur abruptly with changes in  $V_0$  as small as a few millivolts.*

*Note 2: You will need to adjust the gains on the channels as  $V_{\text{in}}$  changes; there is a lot of "back and forth" with controls on the oscilloscope with this exercise.*

**Q.1 Determine the resonance frequency, denoted  $f_0$ , for the circuit using  $V_0 = 10 \text{ mV}$ ; compare with  $1/\sqrt{LC(0)}$ . Take a SCREENSHOT to justify your answer.**

## Q.2 What is the expected phase-shift between $V_{in}$ and $V_{out}$ at resonance?

Switch to the use of the DAC board to record the data and analyze it in Matlab.

## Q.3 Document the transitions to frequency doubling, tripling, quadrupling, and quintupling as "X-Y" and "X-T" plots. Figure 7.2 supplies examples from one experiment, but your details will differ.

## Q.4 Take and report the power spectrum for the case of the lowest subharmonics that you can generate. Label all features.

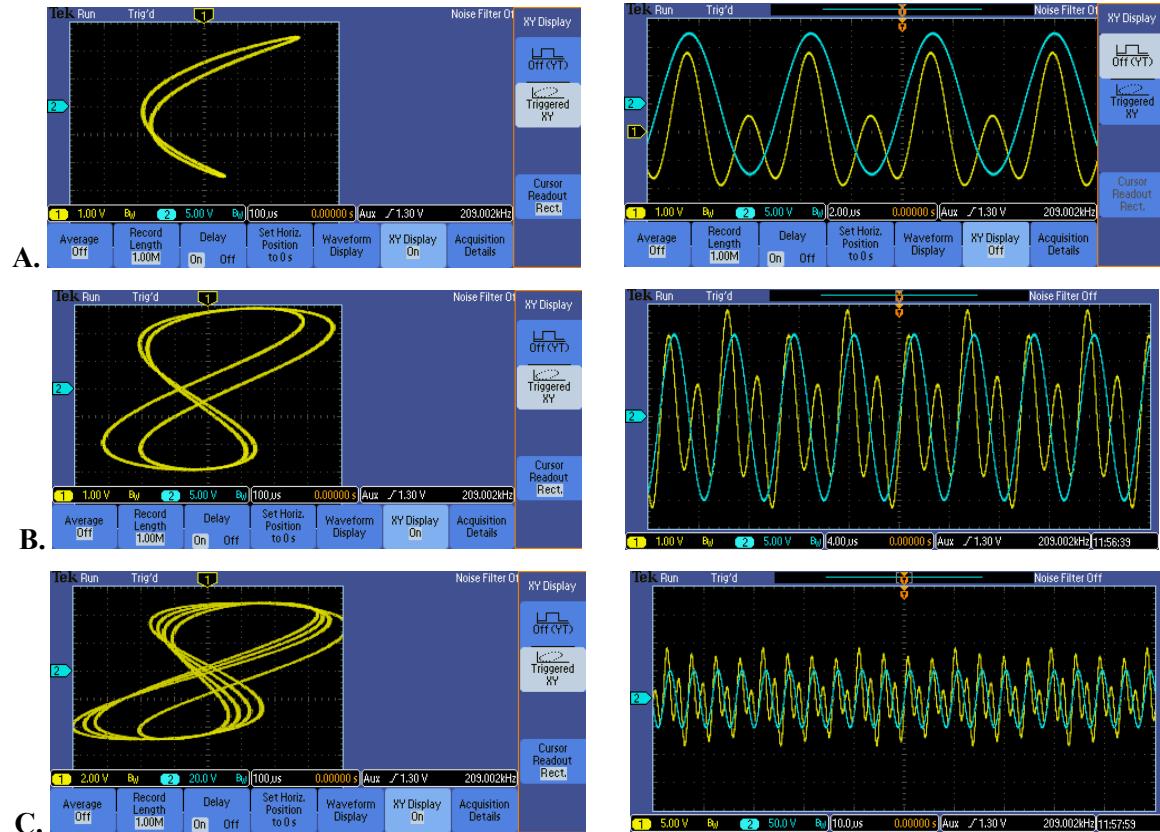


Figure 7.2. Examples of data for  $V_{in}$  and  $V_{out}$ , plotted as "X-Y" and "X-T" (blue trace is  $V_{in}$  and yellow trace is  $V_{out}$ ) when the fundamental of  $V_{out}$  occurs at (A)  $f$ , (B)  $f/2$ , and (C)  $f/4$ . Resonance was at  $f_0 = 179$  kHz. We used  $f = 208$  kHz, and found  $V_0 = 2.50, 5.78, 9.70$ , and  $14.93$  V at the transitions to the 2<sup>nd</sup> through 5<sup>th</sup> subharmonics.


## 7.2 Spectral analysis of human voice

Hook an electret microphone to the input to the DAC (Figure 7.3). We are going to record your voice - speaking, singing, etc., and analyze the frequency content.

The electret sound sensor is capacitive; sound pressure varies the spacing ( $d$ ) and thus capacitance ( $C$ ) between two plates, the charge on the plates is held nearly constant, so the output voltage of the capacitor changes with sound pressure according to  $V = Q/C$  so  $\Delta V \propto \Delta d \propto \Delta(\text{pressure})$  for small deviations. It includes a FET buffer within the microphone package; think of the FET as an infinite resistance input to maintain the charge on the sound




sensor. The FET's output current is converted to a voltage by the  $2.2\text{ k}\Omega$  pull-up resistor, so the output impedance of the microphone is just  $2.2\text{ k}\Omega$ .

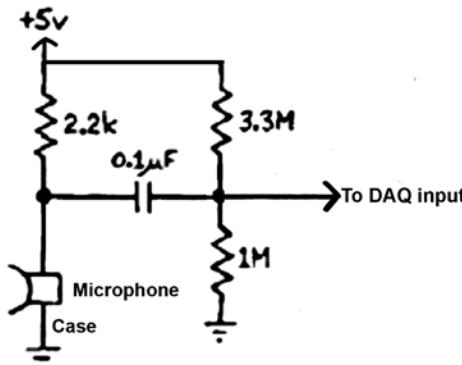

**Figure 7.2:** The microphone has a polarity; the case, connected to one of the pins with a tab, is grounded.

Record a clip of your voice, the time-series, using an acquisition rate of 50 kHz.

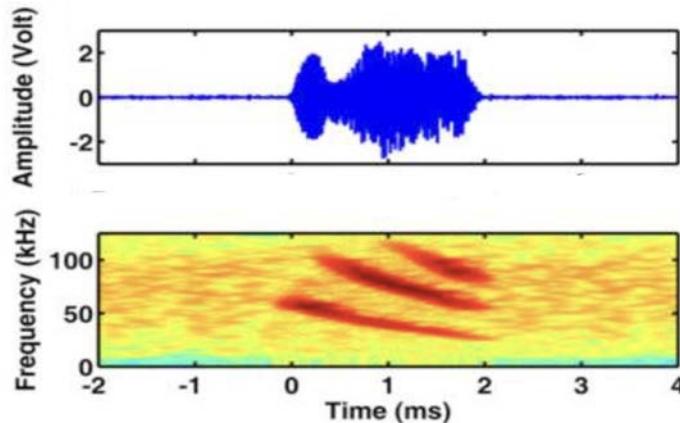**Q.4 Compute the spectrogram - the continuous short-time FFT - of the chirped phonemes "da", "Ba", and "Ga" recorded over a 5 s time-series Provide plots. What do you see?**



**Q.5 Provide 10 to 20 s plots of recordings of continuous speech and the associated spectrogram. What do you see?**

**Q.6 Compute the envelope of the previous recording, defined through a short-time root-mean-square estimate of the time -series - or choose to use a fancy, e.g., Hilbert transform, method. Then take the power of the spectrum, i.e., the second spectrum. What do you see?\**