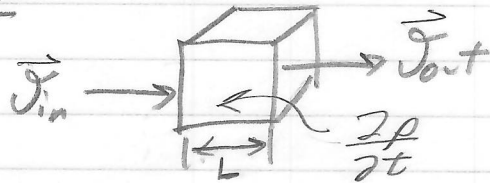


Phys 4L - Lecture 1

Two laws from E&M give rise to electrical circuit analysis

Conservation of charge


$$\vec{\nabla} \cdot \vec{J} = -\frac{\partial \rho}{\partial t}$$



\vec{J} is the current density
with units of $Q/L^2T = Q/L^3 \cdot L/T = \text{charge density} \times \text{velocity}$
 ρ is the charge density
with units of Q/L^3

If charge is not created or destroyed, $\frac{\partial \rho}{\partial t} = 0$ and
 $\vec{\nabla} \cdot \vec{J} = 0$. B.T. by the Divergence Theorem
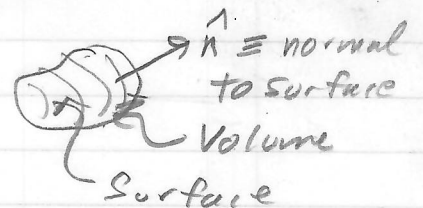
$$\int_{Vol} \vec{\nabla} \cdot \vec{J} d^3r = \int_{Surf} \vec{J} \cdot \hat{n} d^2r$$




$$0 = I_{out} - I_{in}$$

where I is current with units Q/t , In general


$$\sum_i I_i = 0 \text{ at a node}$$

This is Kirchoff's Current Law.

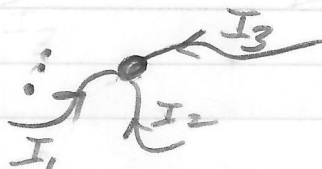

Examples

Current division

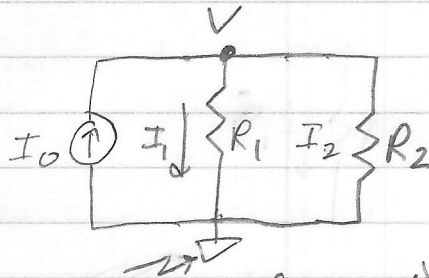

One node can be set to zero (ground)

Sum of currents flowing into node "V"

$$0 = -I_0 + V/R_1 + V/R_2$$

$$V \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = I_0$$


$$V = \frac{R_1 R_2}{R_1 + R_2} I_0$$

$$I_1 = V/R_1 = \frac{R_2}{R_1 + R_2} I_0$$

$$I_2 = \frac{V}{R_2} = \frac{R_1}{R_1 + R_2} I_0$$

Current divides based on conductance $G \equiv 1/R$

Voltage division


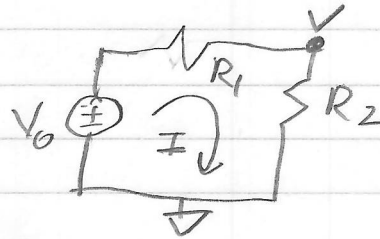


Sum of voltage drops around loop


$$\frac{V - V_0}{R_1} + \frac{V}{R_2} = 0$$


$$V = V_0 \frac{R_2}{R_1 + R_2}$$


Irrelevant Resistors "R_x" - Why?

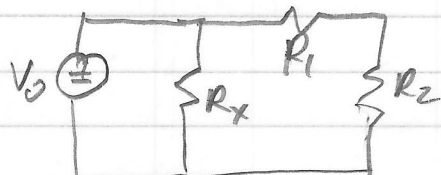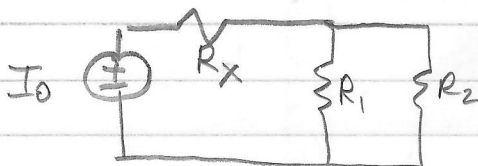

Ideal Sources vs Real Sources

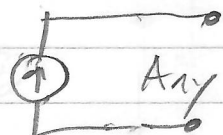I_0  Any voltage can develop in an ideal source.

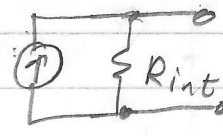I_0  Max of $I_0 R_{int}$ voltage drop because of internal resistance

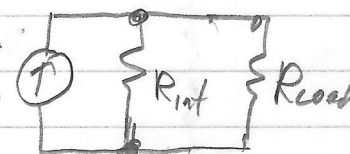I_0  $I_{Load} = \frac{R_{int}}{R_{int} + R_{Load}} I_0$

$\xrightarrow{R_{int} \rightarrow \infty} \frac{I_0}{1 + R_L/R_i} \approx (1 - \frac{R_L}{R_i}) I_0$

When $R_{Load} \rightarrow \infty$, no current flows

$R_{Load} \rightarrow 0$, no voltage drop occurs

Since Power = $I V$, there is an optimal R_L




$$\text{Power} = I_L V_L = I_L^2 R_L = I_0^2 \frac{R_i^2 R_L}{(R_i + R_L)^2}$$

$$\frac{2 \text{Power}}{2 R_L} = I_0 R_i^2 \frac{(R_i^2 - R_L^2)}{(R_i + R_L)^2}$$


$$= 0 \text{ for } R_i = R_L$$

$$\text{Maximum Power in the Load} = \left(\frac{I_0}{2}\right)^2 R_L$$


Equal Division of Current \rightarrow

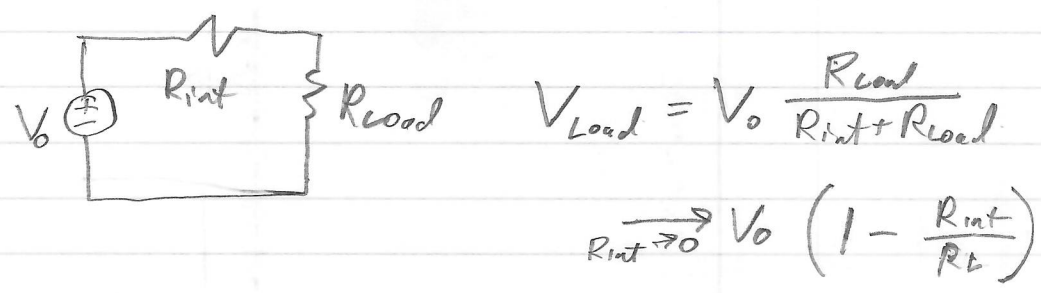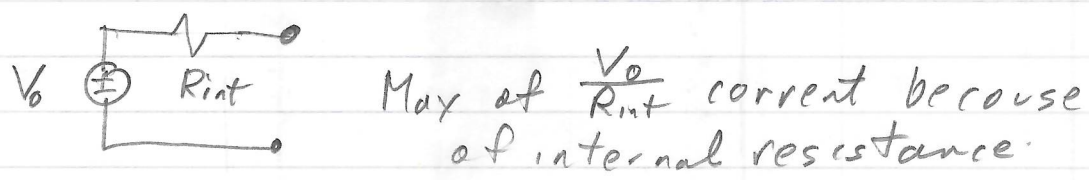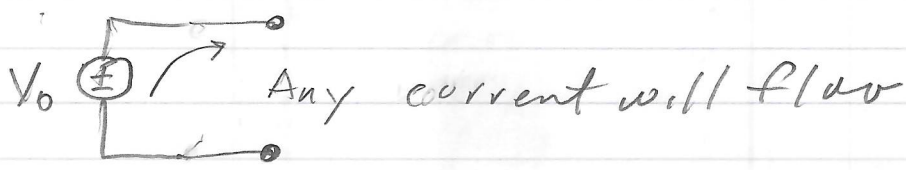

Equivalence of sources

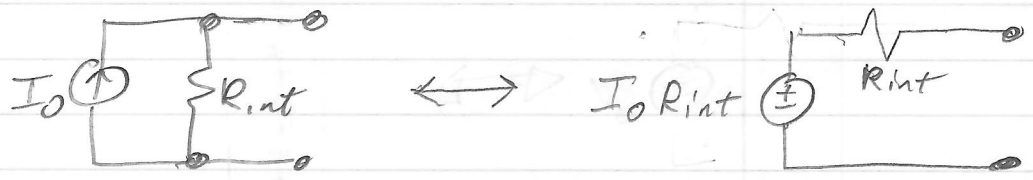

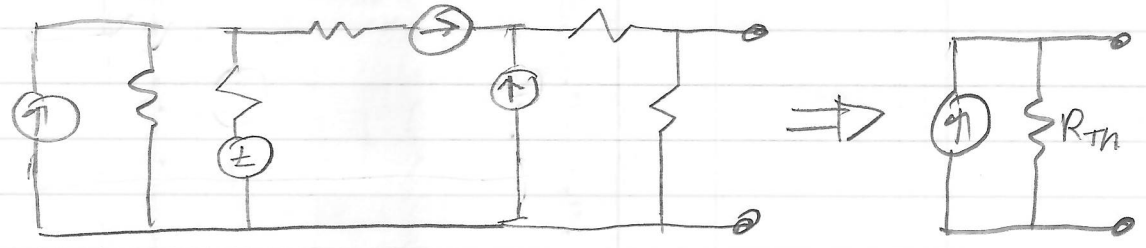
In general, any circuit of resistors, current sources, and voltage sources can be reduced to a "Thevenin" equivalent of one source and one resistor (R_{TH})



- ① Calculate open circuit voltage at output
 OR
- ② Calculate short circuit current at output.

③ Calculate equivalent resistance with current sources as open circuits voltage sources as short circuits

An example

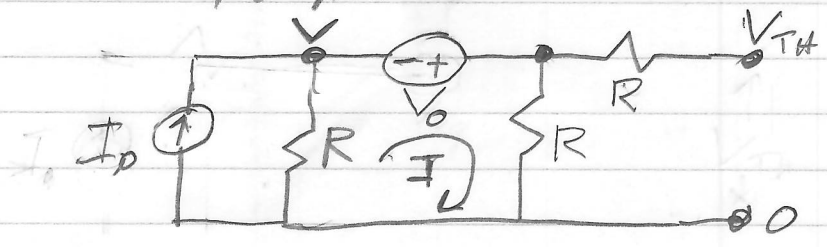


$$-I_0 + \frac{V}{R} + I = 0$$

$$V_{TH} = IR \quad \text{and} \quad V_{TH} = V_0 + V$$

$$\text{and } -I_0 + \frac{V_{TH} - V_0}{R} + \frac{V_{TH}}{R} = 0$$

$$V_{TH} = \frac{I_0 R + V_0}{2}$$

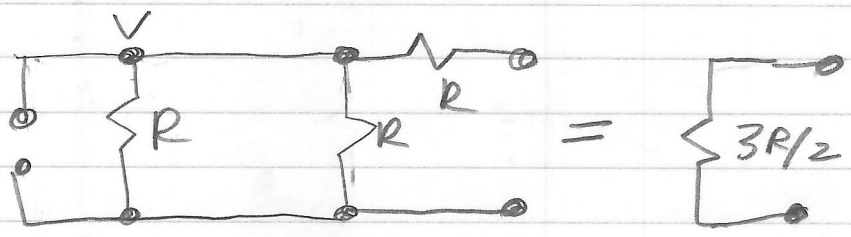

The equivalent circuit is

