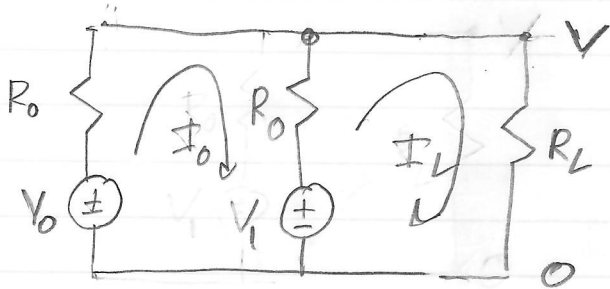


Physics 4L - Lecture 2



First we finish up our analysis of circuits and consider KCL

$$\textcircled{1} -V_0 + R_0 I_0 + R_0 (I_0 - I_L) + V_1 = 0$$

OR

$$2R_0 I_0 - R_0 I_L = V_0 - V_1$$

$$\textcircled{2} -V_1 + R_0 (I_L - I_0) + R_L I_L = 0$$

OR

$$-R_0 I_0 + (R_0 + R_L) I_L = V_1$$

$$\begin{pmatrix} 2R_0 & -R_0 \\ -R_0 & (R_0 + R_L) \end{pmatrix} \begin{pmatrix} I_0 \\ I_L \end{pmatrix} = \begin{pmatrix} V_0 - V_1 \\ V_1 \end{pmatrix}$$

Recall $\begin{pmatrix} a & b \\ c & d \end{pmatrix}^{-1} = \frac{1}{ad - bc} \begin{pmatrix} d & -b \\ -c & a \end{pmatrix}$

$$\begin{pmatrix} I_0 \\ I_L \end{pmatrix} = \frac{1}{R_0(R_0 + 2R_L)} \begin{pmatrix} R_0 + R_L & R_0 \\ R_0 & 2R_0 \end{pmatrix} \begin{pmatrix} V_0 - V_1 \\ V_1 \end{pmatrix}$$

$$I_L = \frac{R_0(V_0 - V_1) + 2R_0 V_1}{R_0(R_0 + 2R_L)} = \frac{V_0 + V_1}{R_0 + 2R_L}$$

$$I_L = \left(\frac{V_0 + V_1}{2} \right) \frac{1}{R_0/2 + R_L}$$


average voltage \uparrow

\uparrow Parallel internal resistances

The voltage across R_L is just

$$V_L = R_L I_L = \left(\frac{V_0 + V_1}{2} \right) \cdot \frac{R_L}{R_0/2 + R_L}$$

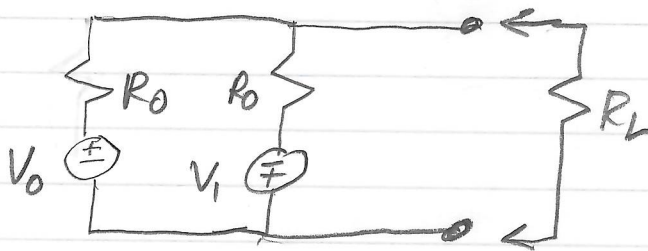We can use this circuit to review Thevenin equivalence. Let's consider




The Thevenin voltage is observed by taking $R_L \rightarrow \infty$. Then

$$\begin{aligned} V_{TH} &= V_{\text{open circuit}} = V_L (R_L \rightarrow \infty) \\ &= \frac{V_0 + V_1}{2} \end{aligned}$$

The Thevenin current is observed by taking $R_L \rightarrow 0$. Then

$$\begin{aligned} I_{TH} &= I_{\text{short circuit}} = I_L (R_L \rightarrow 0) \\ &= \frac{V_0 + V_1}{2} \frac{1}{R_0/2} \end{aligned}$$

$$R_{TH} = V_{TH} / I_{TH} = R_0/2$$

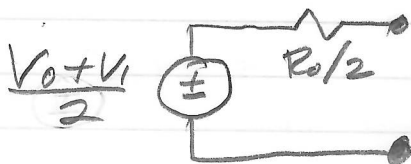


Time dependent components

We now consider the use of circuit elements that have a time dependent relation between current and voltage.

Capacitor


$$Q = C V$$

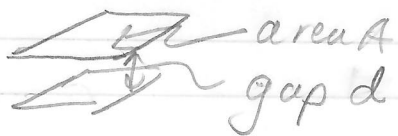Charge = $\int i dt$ Geometry of confined electric field



$$C = \epsilon_0 \epsilon_r \frac{A}{d}$$

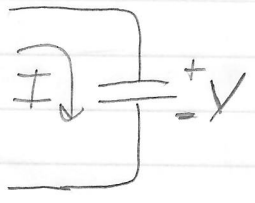
8.9 F/m material, dielectric constant or ease of polarizability



$$V(t) = V(0) + \frac{1}{C} \int_0^t dt' I(t')$$

$Q(t)$

We have $I(t) = C \frac{dV(t)}{dt}$

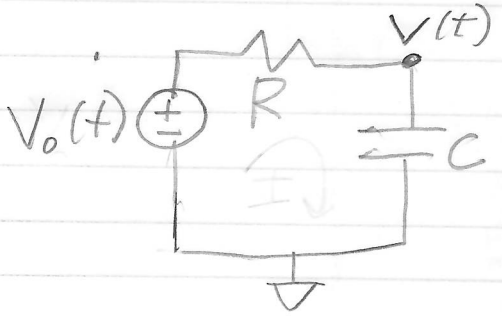

Kirchoff's Voltage Law

$$0 = \frac{V(t) - V_0(t)}{R} + C \frac{dV(t)}{dt}$$

$$(RC) \frac{dV(t)}{dt} + V(t) = V_0(t)$$

The product RC has units of time, the scale for charging the capacitor.


$$\tau \frac{dV(t)}{dt} + V(t) = V_0(t)$$

Inductor

$$\Phi_B = LI$$


Magnetic flux = $\int \vec{B} \cdot \hat{n} d\vec{r}$
 Surface

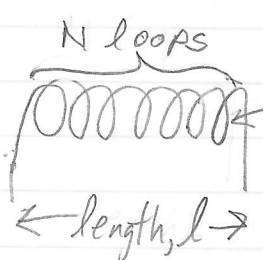Geometry of confined magnetic field lines



$$L = \mu_0 \mu_r \frac{N^2}{l} NA$$

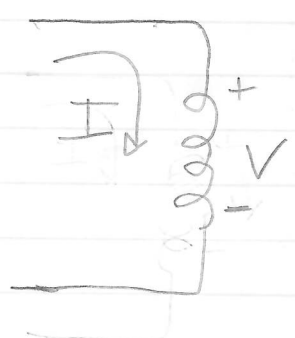
$4\pi \times 10^{-7} \text{ H/m}$ material in core, magnetic permeability or ease of polarizability



$$V(t) = L \frac{dI(t)}{dt}$$

$$I(t) = I_0(0) + \frac{1}{L} \int_0^t dt' V(t')$$

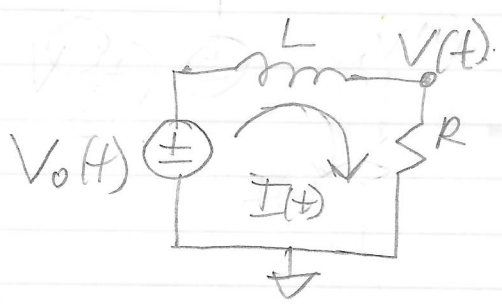$\Phi_B(t)$, recalling $\int \vec{E} \cdot \hat{n} d\vec{r} = -\frac{d}{dt} \Phi_B$



$$0 = -V_0(t) + L \frac{dI(t)}{dt} + I(t)R$$

$$V(t) = I(t)R$$

$$\frac{L}{R} \frac{dV(t)}{dt} + V(t) = V_0(t)$$

like RC circuit but with a time constant $\tau = L/R$

In both cases, we need to solve the equation

$$\tau \frac{dV(t)}{dt} + V(t) = V_0(t)$$

for an arbitrary input $V_0(t)$.

What is the special role of " τ "?

If we consider the homogeneous equation

$$\tau \frac{dV(t)}{dt} + V(t) = 0$$

$$\text{we have } \int_{V(0)}^{V(t)} \frac{dV'}{V'} = \frac{-1}{\tau} \int_0^t dt'$$

$$\ln \frac{V(t)}{V(0)} = -t/\tau$$

$$V(t) = V_0 e^{-t/\tau}$$

τ sets the scale for time.